

# ELECTRICAL CIRCUIT ANALYSIS LAB

## II B.Tech-I SEMESTER

### STUDENT OBSERVATION RECORD



## DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING

**VEMU INSTITUTE OF TECHNOLOGY::P.KOTHAKOTA**

NEAR PAKALA, CHITTOOR-517112

(Approved by AICTE, New Delhi & Affiliated to JNTUA, Anantapuramu)

## **VEMU INSTITUTE OF TECHNOLOGY**

### **DEPT.OF ELECTRICAL AND ELECTRONICS ENGINEERING**

#### **VISION OF THE INSTITUTE**

- ✚ To be a premier institute for professional education producing dynamic and vibrant force of technocrats with competent skills, innovative ideas and leadership qualities to serve the society with ethical and benevolent approach.

#### **MISSION OF THE INSTITUTE**

- ✚ To create a learning environment with state-of-the art infrastructure, well equipped laboratories, research facilities and qualified senior faculty to impart high quality technical education.
- ✚ To facilitate the learners to foster innovative ideas, inculcate competent research and consultancy skills through Industry-Institute Interaction.
- ✚ To develop hard work, honesty, leadership qualities and sense of direction in rural youth by providing value based education.

#### **VISION OF THE DEPARTMENT**

- ✚ To produce professionally deft and intellectually adept Electrical and Electronics Engineers and equip them with the latest technological skills, research & consultancy competencies along with social responsibility, ethics, Lifelong Learning and leadership qualities.

#### **MISSION OF THE DEPARTMENT**

- ✚ To produce competent Electrical and Electronics Engineers with strong core knowledge, design experience & exposure to research by providing quality teaching and learning environment.
- ✚ To train the students in emerging technologies through state - of - the art laboratories and thus bridge the gap between Industry and academia.
- ✚ To inculcate learners with interpersonal skills, team work, social values, leadership qualities and professional ethics for a holistic engineering professional practice through value based education.

## PROGRAM EDUCATIONAL OBJECTIVES(PEOs)

Programme Educational Objectives (PEOs) of B.Tech (Electrical and Electronics Engineering) program are:

Within few years of graduation, the graduates will

**PEO 1:** Provide sound foundation in mathematics, science and engineering fundamentals to analyze, formulate and solve complex engineering problems.

**PEO 2:** Have multi-disciplinary Knowledge and innovative skills to design and develop Electrical & Electronics products and allied systems.

**PEO 3:** Acquire the latest technological skills and motivation to pursue higher studies leading to research.

**PEO 4:** Possess good communication skills, team spirit, ethics, modern tools usage and the life-long learning needed for a successful professional career.

### PROGRAM OUTCOMES (POs)

PO-1	<b>Engineering knowledge:</b> Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
PO-2	<b>Problem analysis:</b> Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
PO-3	<b>Design/development of solutions:</b> Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
PO-4	<b>Conduct investigations of complex problems:</b> Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
PO-5	<b>Modern tool usage:</b> Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.
PO-6	<b>The engineer and society:</b> Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
PO-7	<b>Environment and sustainability:</b> Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
PO-8	<b>Ethics:</b> Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
PO-9	<b>Individual and team work:</b> Function effectively as an individual, and as a member or leader

	in diverse teams, and in multidisciplinary settings.
<b>PO-10</b>	<b>Communication:</b> Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
<b>PO-11</b>	<b>Project management and finance:</b> Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.
<b>PO-12</b>	<b>Life-long learning:</b> Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

### **PROGRAM SPECIFIC OUTCOMES (PSOs)**

On completion of the B.Tech. (Electrical and Electronics Engineering) degree, the graduates will be able to

**PSO-1: Higher Education:** Apply the fundamental knowledge of Mathematics, Science, Electrical and Electronics Engineering to pursue higher education in the areas of Electrical Circuits, Electrical Machines, Electrical Drives, Power Electronics, Control Systems and Power Systems.

**PSO-2: Employment:** Get employed in Public/Private sectors by applying the knowledge in the domains of design and operation of Electronic Systems, Microprocessor based control systems, Power systems, Energy auditing etc.

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY ANANTAPUR****II B.Tech. I-Sem (EEE)****ELECTRICAL CIRCUIT ANALYSIS LABORATORY(20A02301P)****COURSE OUTCOMES**

C216.1	Analyze & Experimentally verify various resonance phenomenon
C216.2	Analyze various current locus diagrams.
C216.3	Apply and experimentally analyze two port network parameters
C216.4	Analysis of R, RL and RLC circuits with different excitations
C216.5	Simulate the DC & AC Circuits



**Name:** \_\_\_\_\_

**H.T.No:** \_\_\_\_\_

**Year/Semester:** \_\_\_\_\_

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY ANANTAPUR****B. Tech II-I Sem. (EEE)****L T P C****0 0 3 1.5****(20A02301P) ELECTRICAL CIRCUIT ANALYSIS LABORATORY**

**The following experiments are required to be conducted as compulsory experiments:**

1. Locus Diagram of RL Series Circuits:
  - a) Variable 'R' and Fixed 'L' b) Variable 'L' and Fixed 'R'
2. Locus Diagram of RC Series Circuits:
  - a) Variable 'R' and Fixed 'C' b) Variable 'C' and Fixed 'R'
3. Series Resonance
4. Parallel Resonance
5. Determination of Z Parameters
6. Determination of Y Parameters
7. Transmission Parameters
8. Hybrid Parameters
9. Determination of Coefficient of coupling
10. Response Analysis of R, RL and RLC circuits with sinusoidal and non-sinusoidal excitations.

**ADDITIONAL EXPERIENTS**

11. Simulation of DC Circuits
12. Simulation of AC Circuits

**VEMU INSTITUTE OF TECHNOLOGY::P.KOTHAKOTA**

NEAR PAKALA, CHITTOOR-517112

(Approved by AICTE, New Delhi &amp; Affiliated to JNTUA, Anantapuramu)

**List of Experiments to be conducted****ELECTRICAL CIRCUIT ANALYSIS LABORATORY**

S.NO.	NAME OF THE EXPERIMENT
1	Locus Diagram of RL Series Circuits: a) Variable 'R' and Fixed 'L' b) Variable 'L' and Fixed 'R'
2	Locus Diagram of RC Series Circuits: a) Variable 'R' and Fixed 'C' b) Variable 'C' and Fixed 'R'
3	Series Resonance
4	Parallel Resonance
5	Determination of Z Parameters
6	Determination of Y Parameters
7	Transmission Parameters
8	Hybrid Parameters
9	Determination of Coefficient of coupling
10	Response Analysis of R, RL and RLC circuits with sinusoidal and non-sinusoidal excitations
<b>Additional Experiments</b>	
11	Simulation of DC Circuits
12	Simulation of AC Circuits

**VEMU INSTITUTE OF TECHNOLOGY::P.KOTHAKOTA**

NEAR PAKALA, CHITTOOR-517112

(Approved by AICTE, New Delhi &amp; Affiliated to JNTUA, Anantapuramu)

**List of Experiments to be conducted****CONTENTS****ELECTRICAL CIRCUIT ANALYSIS LABORATORY**

<b>S.NO.</b>	<b>NAME OF THE EXPERIMENT</b>	<b>PAGE NO.</b>
1	Locus Diagram of RL Series Circuits: a) Variable 'R' and Fixed 'L' b) Variable 'L' and Fixed 'R'	
2	Locus Diagram of RC Series Circuits: a) Variable 'R' and Fixed 'C' b) Variable 'C' and Fixed 'R'	
3	Series Resonance	
4	Parallel Resonance	
5	Determination of Z Parameters	
6	Determination of Y Parameters	
7	Transmission Parameters	
8	Hybrid Parameters	
9	Determination of Coefficient of coupling	
10	Response Analysis of R, RL and RLC circuits with sinusoidal and non-sinusoidal excitations	
<b>Additional Experiments</b>		
11	Simulation of DC Circuits	
12	Simulation of AC Circuits	

**GENERAL INSTRUCTIONS FOR LABORATORY CLASSES****DO'S**

1. Without Prior permission do not enter into the Laboratory.
2. While entering into the LAB students should wear their ID cards.
3. The Students should come with proper uniform.
4. Students should sign in the LOGIN REGISTER before entering into the laboratory.
5. Students should come with observation and record note book to the laboratory.
6. Students should maintain silence inside the laboratory.
7. Circuit connections must be checked by the lab-in charge before switching the supply

**DONT'S**

8. Students bringing the bags inside the laboratory..
9. Students wearing slippers/shoes insides the laboratory.
10. Students scribbling on the desk and mishandling the chairs.
11. Students using mobile phones inside the laboratory.
12. Students making noise inside the laboratory.
13. Students mishandle the devices.
14. Students write anything on the devices

**ELECTRICAL CIRCUIT ANALYSIS LABORATORY****SCHEME OF EVALUATION**

S.No	Experiment Name	Date	Marks Awarded				Total 30(M)
			Record (10M)	Observation (10M)	Viva Voce (5M)	Attendance (5M)	
1	Locus Diagram of RL Series Circuits: a) Variable 'R' and Fixed 'L' b) Variable 'L' and Fixed 'R'						
2	Locus Diagram of RC Series Circuits: a) Variable 'R' and Fixed 'C' b) Variable 'C' and Fixed 'R'						
3	Series Resonance						
4	Parallel Resonance						
5	Determination of Z Parameters						
6	Determination of Y Parameters						
7	Transmission Parameters						
8	Hybrid Parameters						
9	Determination of Coefficient of coupling						
10	Response Analysis of R, RL and RLC circuits with sinusoidal and non-sinusoidal excitations						
<b>ADDITIONAL EXPERIENTS</b>							
11	Simulation of DC Circuits						
12	Simulation of AC Circuits						

**Signature of Lab In-charge**

EXP.NO:1

DATE:

**01.Locus Diagram of RL Series Circuits:****a) Variable 'R' and Fixed 'L' b) Variable 'L' and Fixed 'R'**

**AIM:** To design the Locus Diagram of RL Series Circuits for the given circuit.

**AIM:** To draw the current locus diagrams for series RL and RC circuits by varying resistance and for series RC circuit by varying capacitance.

**APPARATUS:**

S. No	Name of the apparatus	Range	Type	Quantity
1	Signal generator	(0 – 3M)Hz, (0-20)V <sub>PP</sub>	-	1No
2	Decade Resistance Box	(0-111.11K)Ω	-	1No
3	Decade inductance Box	(0-1.11)H	-	1No
4	Decade Capacitance Box	(0-1.11)F	-	1No
5	Ammeter	(0-10m)A	MC	1No
6	Connecting wires	-	-	Required number

**PROCEDURE:****Series RL circuit( Varying resistance (R) and Fixed Inductance L)**

1. Set the signal generator to be in sine wave mode and adjust the output voltage to 20V peak to peak, frequency to 200 Hzs.
2. Connect the circuit as per fig.
3. Vary the resistance in the circuit using DRB in steps and note down the current through the circuit for each step(ammeter reading).
4. Calculate phase angle  $\phi$  using to formula  $\phi = \tan^{-1} \left( \frac{X_L}{R} \right)$  for each step.
5. Disconnect the circuit.
6. Plot the current locus diagram by taking current on x axis and voltage on Y – axis.

**Series RL circuit( Varying Inductance (L) and Fixed Resistance R)**



1. Set the signal generator to be in sine wave mode and adjust the output voltage to 20V peak to peak, frequency to 200 Hzs.
2. Connect the circuit as per fig.
3. Vary the Inductance in the circuit using DLB in steps and note down the current through the circuit for each step (ammeter reading).
4. Calculate phase angle  $\phi$  using to formula  $\phi = \tan^{-1}$  for each step.
5. Disconnect the circuit.
6. Plot the current locus diagram by taking current on x axis and voltage on Y – axis.

**PRECAUTIONS:**

1. Set the ammeter pointer at zero position.
2. Take the readings with out parallax error.
3. Avoid loose connections.


**CURRENT LOCUS DIAGRAMS****GIVEN CIRCUIT**

Series RL circuit (R Varying)

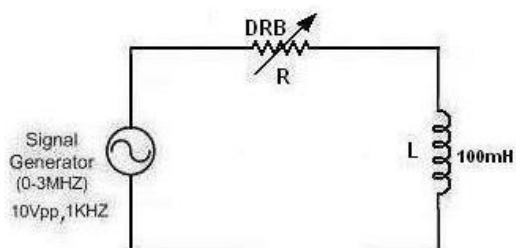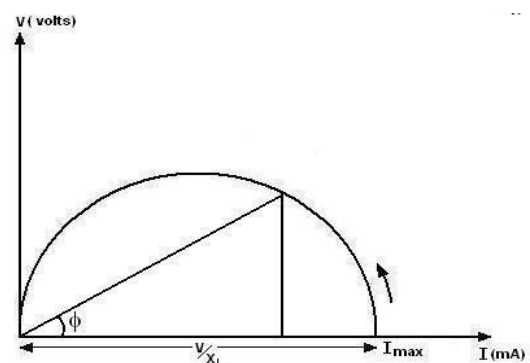**MODEL GRAPH**

S.NO	R(ohms)	I(mA)	$\Phi = \tan^{-1}\left(\frac{X_L}{R}\right)$

Series RL circuit (L Varying & R Fixed)

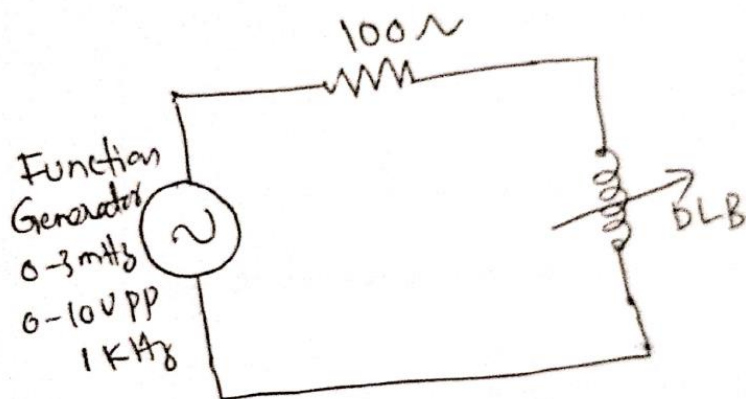

S.NO	R (ohms)	L	I(mA)	$\Phi = \tan^{-1}\left(\frac{X_L}{R}\right)$

Theoretical Circuit diagram:

Practical circuit diagram:

Fig

**RESULT:**

The current locus diagrams for series RL circuits by varying resistance and by varying Capacitance are drawn.

**CONCLUSION:**

The current locus diagrams of series RL and RC circuits with resistance varying and for series RC circuit with capacitance varying are semi-circles.

**EXP.NO:02****DATE:**

**02.Locus Diagram of RC Series Circuits:****a) Variable 'R' and Fixed 'C' b) Variable 'C' and Fixed 'R'**

**AIM:** To draw the current locus diagrams for series RC circuits by varying resistance and for series RC circuit by varying capacitance.

**APPARATUS:**

S. No	Name of the apparatus	Range	Type	Quantity
1	Signal generator	(0 – 3M)Hz, (0-20)V <sub>PP</sub>	-	1No
2	Decade Resistance Box	(0-111.11K) $\Omega$	-	1No
3	Decade inductance Box	(0-1.11)H	-	1No
4	Decade Capacitance Box	(0-1.11)F	-	1No
5	Ammeter	(0-10m)A	MC	1No
6	Connecting wires	-	-	Required number

**PROCEDURE:**

**Series RC circuit( varying resistance )**

1. Set the signal generator to be in sine wave mode and adjust the output voltage to 20V peak to peak, frequency to 200 Hzs.
2. Connect the circuit as per fig.
3. Vary the resistance in the circuit using DRB in steps and note down the current through the circuit for each step(ammeter reading).
4. Calculate phase angle  $\phi$  using to formula  $\phi = \tan^{-1} \left( \frac{X_C}{R} \right)$  for each step.
5. Disconnect the circuit.
6. Plot the current locus diagram by taking current on Y axis and voltage on X – axis.

**Series RC circuit( varying capacitance )**

1. Set the signal generator to be in sine wave mode and adjust the output voltage to 20V peak to peak, frequency to 200 Hzs.
2. Connect the circuit as per fig.
3. Vary the Capacitance in the circuit using DCB in steps and note down the current through the circuit for each step(ammeter reading).



4. Calculate phase angle  $\phi$  using to formula  $\phi = \tan^{-1} \left( \frac{X_C}{R} \right)$  for each step.
5. Disconnect the circuit.
6. Plot the current locus diagram by taking current on Y axis and voltage on X – axis.

**PRECAUTIONS:**



1. Set the ammeter pointer at zero position.
2. Take the readings with out parallax error.
3. Avoid loose connections.



**CURRENT LOCUS DIAGRAMS****GIVEN CIRCUIT****MODEL GRAPH**

Series RC circuit (C Varying)

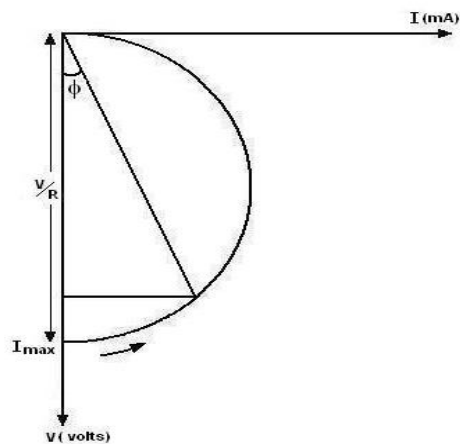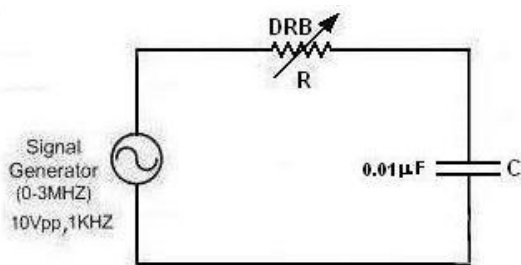

Series RC circuit (C Varying)

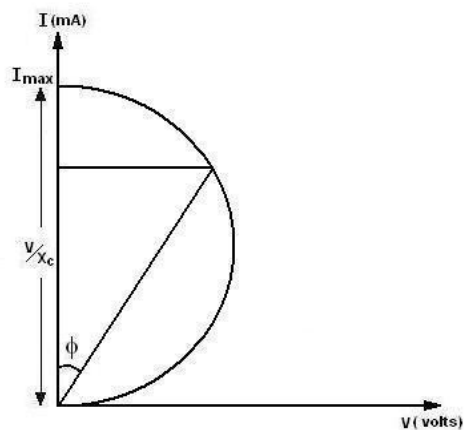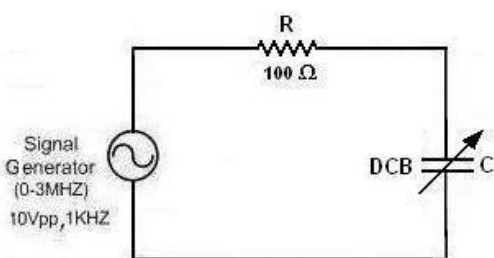

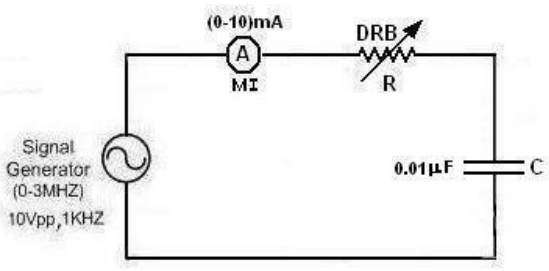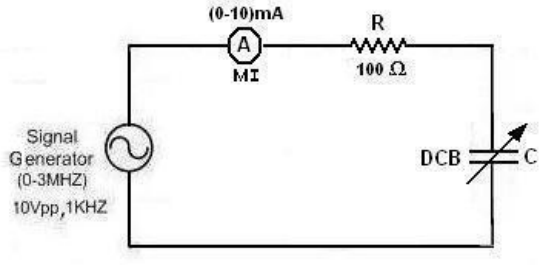Theoretical Circuit diagram:	Practical circuit diagram:																
	<div style="text-align: right; margin-bottom: 5px;">I</div>  <p style="text-align: center;"><b>Fig</b></p> <table border="1" style="width: 100%; border-collapse: collapse; margin-bottom: 10px;"> <thead> <tr> <th style="width: 15%;">S.NO</th> <th style="width: 20%;">R(ohms)</th> <th style="width: 15%;">I(mA)</th> <th style="width: 50%;"><math>\Phi = \tan^{-1} \left( \frac{X_C}{R} \right)</math></th> </tr> </thead> <tbody> <tr> <td style="height: 30px;"></td> <td></td> <td></td> <td></td> </tr> </tbody> </table>  <p style="text-align: center;"><b>Fig</b></p> <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 15%;">S.NO</th> <th style="width: 20%;">C(µF)</th> <th style="width: 15%;">I(mA)</th> <th style="width: 50%;"><math>\Phi = \tan^{-1} \left( \frac{X_C}{R} \right)</math></th> </tr> </thead> <tbody> <tr> <td style="height: 30px;"></td> <td></td> <td></td> <td></td> </tr> </tbody> </table>	S.NO	R(ohms)	I(mA)	$\Phi = \tan^{-1} \left( \frac{X_C}{R} \right)$					S.NO	C(µF)	I(mA)	$\Phi = \tan^{-1} \left( \frac{X_C}{R} \right)$				
S.NO	R(ohms)	I(mA)	$\Phi = \tan^{-1} \left( \frac{X_C}{R} \right)$														
S.NO	C(µF)	I(mA)	$\Phi = \tan^{-1} \left( \frac{X_C}{R} \right)$														

**RESULT:**

The current locus diagrams for series RC circuits by varying resistance and for series RC circuit by varying capacitance are drawn.

**CONCLUSION:**

The current locus diagrams of series RC circuits with resistance varying and for series RC circuit with capacitance varying are semi-circles.

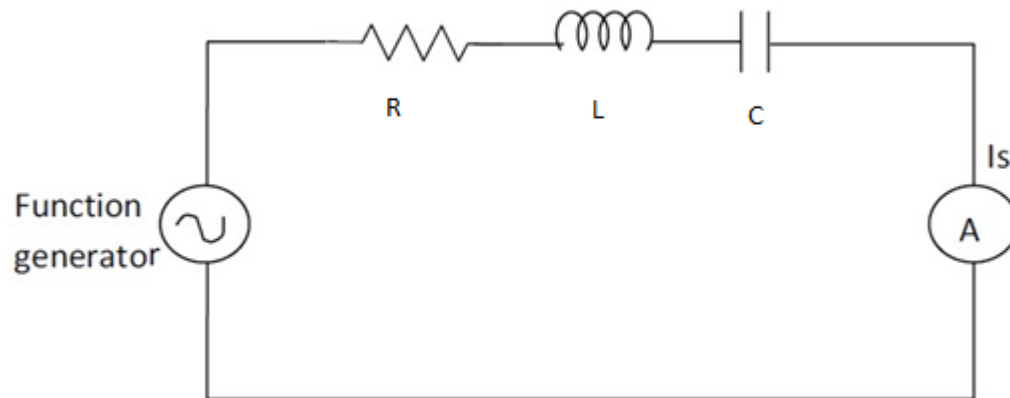
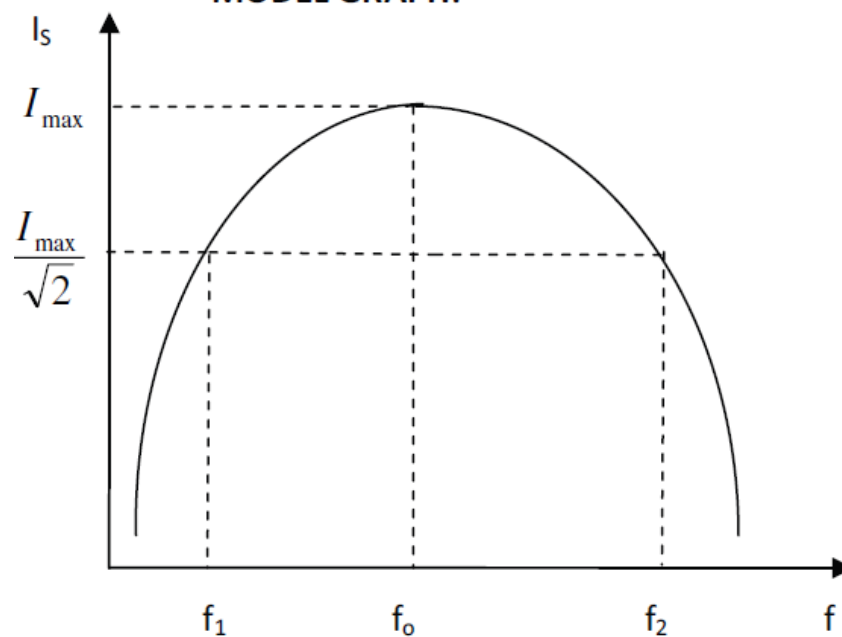
**CIRCUIT DIAGRAM OF SERIES RESONANCE:**

Fig-1

**MODEL GRAPH:**

EXP.NO:03

DATE:

**FREQUENCY RESPONSE OF SERIES RESONANCE CIRCUIT**

**AIM:** To verify resonant frequency, bandwidth & quality factor of RLC series Resonant circuits.

**APPARATUS:**

S. No	Name of the apparatus	Range	Type	Quantity
1	Signal generator	(0 – 3M)Hz, (0-20) V <sub>PP</sub>	-	1No
2	Decade inductance Box	(0-1.11H)	-	1No
3	Decade Capacitance Box	(0-1.11F)	-	1No
4	Decade Resistance Box	(0-111.11K) $\Omega$	-	1No
5	Resistors	1k $\Omega$	Carbon Composition	2No
6	Ammeter	(0-10m) A	MI	1No
7	Bread board	-	-	1No
8	Connecting wires	-	-	Required Number

**PROCEDURE:****Series Resonant circuit**

1. Set the signal generator in sine wave mode.
2. Using C.R.O set the output voltage of the signal generator to an appropriate value (Say 20 V peak to peak).
3. Connect the circuit as per fig (1.1).
4. Vary the frequency of the input signal in steps and note down the corresponding current through the circuit and tabulate the readings.


5. Reduce the frequency to zero.
6. Now decrease the resistance to  $500\ \Omega$  and repeat the steps 4 and 5.
7. Reduce the signal generator voltage to  $0V$  and switch off the supply.
8. Disconnect the circuit and plot the graph by relating dependent and independent variables.
9. The frequency corresponding to maximum current will be the resonant frequency.
10. Draw a line parallel to X-axis, corresponding to  $0.707 I_{\max}$ , which cuts the curve at two points.
11. The frequencies corresponding to those points are called as cut-off frequencies.
12. The difference between lower and upper cut-off frequencies gives the bandwidth.

### **PRECAUTIONS:**


1. Keep the output voltage of the signal generator in zero volt position.
2. Set the ammeter pointer at zero position.
3. Take the readings with out parallax error.
4. Avoid loose connections.

## **SERIES RESONANCE**

GIVEN CIRCUIT

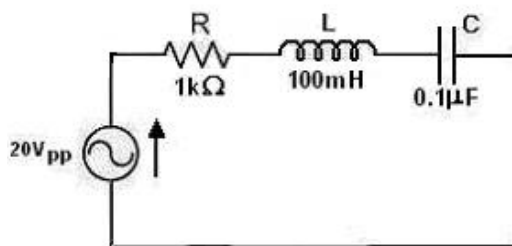

MODEL GRAPH

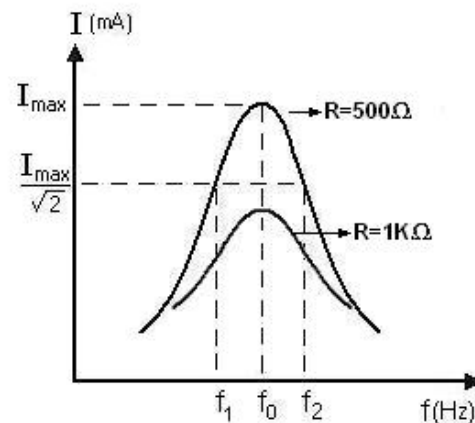

**Theoretical Circuit diagram:**

**Practical circuit diagram:**

Resonant frequency,  $f_0 = \frac{1}{2\pi\sqrt{LC}}$ .

Quality factor,  $Q = \frac{\omega L}{R} = \frac{1}{\omega CR} = \frac{1}{R} \sqrt{\frac{L}{C}} = 1$

Band width =

Resonant frequency,  $f_0 =$

Lower cut-off frequency,  $f_1 =$

Upper cut-off frequency,  $f_2 =$

Band width =  $f_2 - f_1 =$

Quality factor,  $Q = \frac{f_0}{f_2 - f_1}$

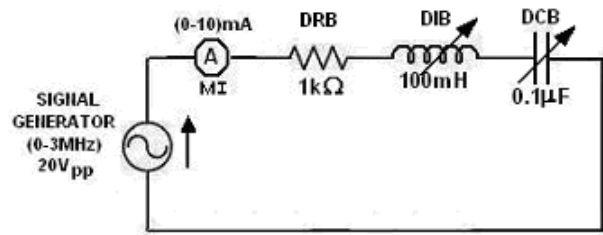


Fig (1.1)

**Tabular Column:**

When R = 1KΩ

S. No	Frequency, f (Hz)	Current, I (mA)

When R = 500Ω

S. No	Frequency, f (Hz)	Current, I (mA)

**RESULT:**

The resonant frequency, bandwidth and quality factor of the given series and parallel resonant circuits are determined and compared with the theoretical values.



S.No	Parameter	Series Resonant circuit	
		Theoretical Values	Practical Values
1	Resonant Frequency, $f_0$		
2	Band width		
3	Quality factor		

**CONCLUSIONS:**

1. Since the current at resonance is maximum, the series resonant circuit is called as acceptor circuit.
2. As the resistance of the circuit decreases, the Q-factor increases and selectivity of the circuit will be better.
3. Since the current at resonance is minimum, the parallel resonant circuit is called as rejector circuit.
4. The variation of the resistance does not affect the resonant frequency.

**VIVA QUESTIONS:-**

- 1) Define Resonance?
- 2) Define bandwidth?
- 3) What is resonant condition in series RLC circuit?
- 4) Define quality factor?
- 5) What is half power frequencies?
- 6) What is the resonance frequency of series RLC circuit?
- 7) What is the band width of series RLC circuit?
- 8) What are the half power frequencies of series RLC circuit?

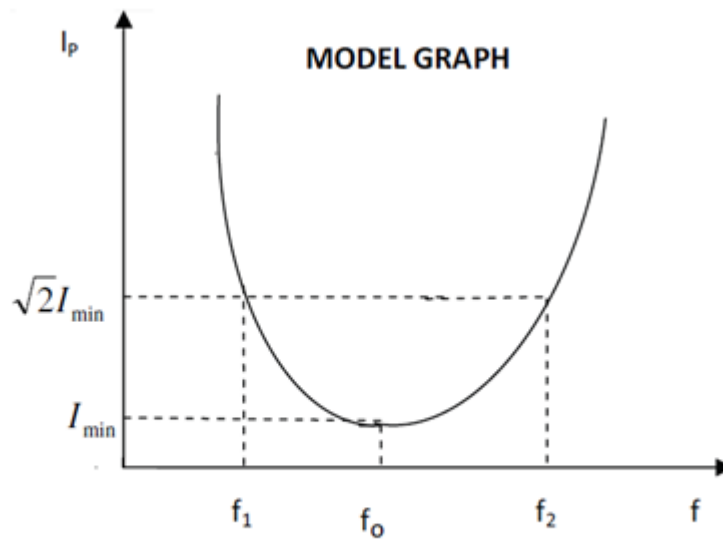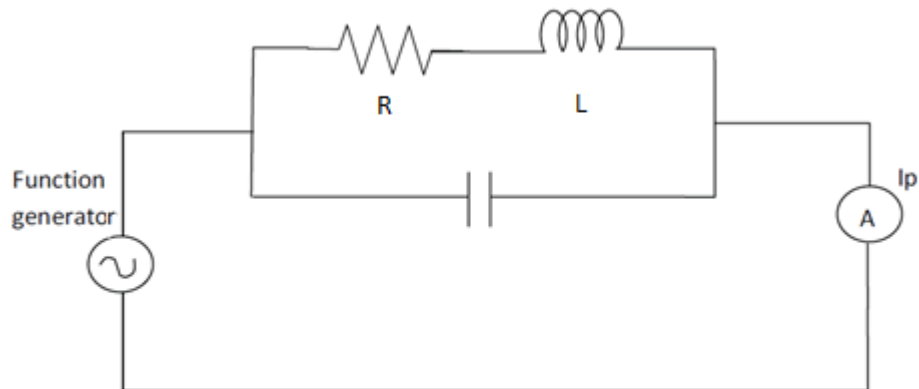**Circuit Diagram:**

EXP.NO:04

DATE:

**ANALYSIS OF PARALLEL RESONANCE CIRCUIT****AIM:** To verify resonant frequency, bandwidth & quality factor of RLC parallel Resonant circuits.**APPARATUS:**

S. No	Name of the apparatus	Range	Type	Quantity
1	Signal generator	(0 – 3M)Hz, (0-20) V <sub>PP</sub>	-	1No
2	Decade inductance Box	(0-1.1H)	-	1No
3	Decade Capacitance Box	(0-1.1F)	-	1No
4	Decade Resistance Box	(0-111.11K) $\Omega$	-	1No
5	Resistors	1k $\Omega$	Carbon Composition	2No
6	Ammeter	(0-10m) A	MI	1No
7	Bread board	-	-	1No
8	Connecting wires	-	-	Required Number

**PROCEDURE:****Resonance in parallel RLC circuit**

1. Connect the circuit as per fig .
2. Vary the frequency of the input signal in steps and note down the corresponding current through the circuit and tabulate the readings.
3. Reduce the frequency to zero.
4. Now decrease the resistance to 500  $\Omega$  and repeat the steps 4 and 5.
5. Reduce the signal generator voltage to 0V and switch off the supply.
6. The frequency corresponding to minimum current will be the resonant frequency.

7. Draw a line parallel to X-axis, corresponding to  $1.414 I_{\min}$ , which cuts the curve at two points.
8. The difference between lower and upper cut-off frequencies gives the bandwidth.

### PRECAUTIONS:

1. Keep the output voltage of the signal generator in zero volt position.
2. Set the ammeter pointer at zero position.
3. Take the readings with out parallax error.
4. Avoid loose connections.

## SERIES RESONANCE



GIVEN CIRCUIT

MODEL GRAPH

PARALLEL RESONANCE

GIVEN CIRCUIT:

MODEL GRAPH:

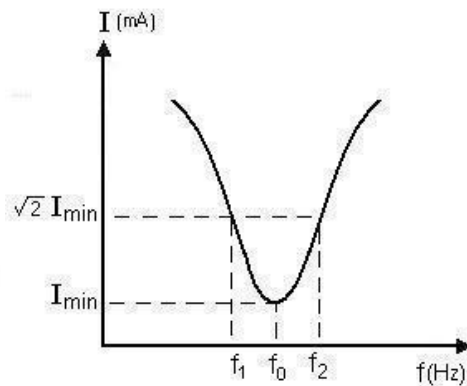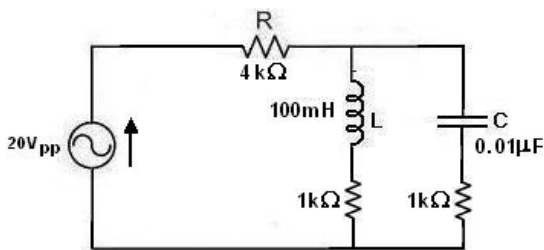

Theoretical Circuit diagram:

Practical circuit diagram:

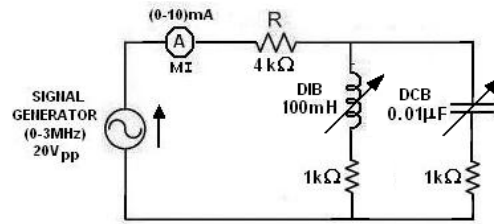
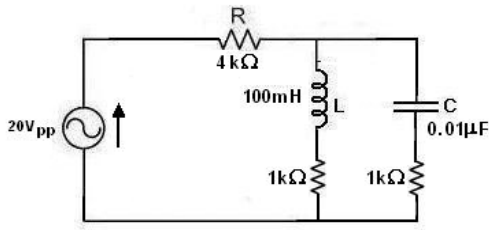


Fig (1.2)

Resonant frequency,  $f_0$ ,

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{CR_L^2 - L}{CR_C^2 - L}}$$

$$\because R_L = R_C, f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Quality factor,  $Q =$

Band width =

Tabular Column:

S. No	Frequency, f (Hz)	Current, I(mA)

$$f_0 = \quad f_1 = \quad f_2 =$$

$$\text{Band width} = f_2 - f_1 =$$

$$Q = \frac{f_0}{f_2 - f_1} =$$

**RESULT:**

S.No	Parameter	Parallel Resonant circuit

The resonant frequency, factor of the given resonant circuits are compared with the

		Theoretical Values	Practical Values
1	Resonant Frequency, $f_0$		
2	Band width		
3	Quality factor		

bandwidth and quality series and parallel determined and theoretical values.

### CONCLUSIONS:

1. Since the current at resonance is maximum, the series resonant circuit is called as acceptor circuit.
2. As the resistance of the circuit decreases, the Q-factor increases and selectivity of the circuit will be better.
3. Since the current at resonance is minimum, the parallel resonant circuit is called as rejector circuit.
4. The variation of the resistance does not affect the resonant frequency.

### VIVA QUESTIONS:-

- 1) Define Resonance?
- 2) What is the quality factor of parallel RLC circuit?
- 3) What is Resonant condition in series RLC circuit?
- 4) Define quality factor?
- 5) What is half power frequencies?

- 6) What is the resonance frequency of parallel RLC circuit?
- 7) What is the band width of parallel RLC circuit?
- 8) What are the half power frequencies of parallel RLC circuit?

**EXPT NO: 05****DATE:****DETERMINATION OF Z PARAMETERS**

**AIM:** To determine open circuit impedance parameters ( $Z$ ) of the given two port network.

**BRIEF THEORY:** In  $Z$  parameters of a two-port, the input & output voltages  $V_1$  &  $V_2$  can be expressed in terms of input & output currents  $I_1$  &  $I_2$ . Out of four variables (i.e  $V_1$ ,  $V_2$ ,  $I_1$ ,  $I_2$ )  $V_1$  &  $V_2$  are dependent variables whereas  $I_1$  &  $I_2$  are independent variables. Thus,

$$V_1 = Z_{11}I_1 + Z_{12} I_2 \quad (1)$$

$$V_2 = Z_{21}I_1 + Z_{22} I_2 \quad (2)$$

Here  $Z_{11}$  &  $Z_{22}$  are the input & output driving point impedances while  $Z_{12}$  &  $Z_{21}$  are the reverse & forward transfer impedances.

**APPARATUS:**

S. No	Name of the apparatus	Range	Type	Quantity
1	Dual channel Regulated power supply	(0 – 30)V	-	1
2	Voltmeters	(0-10) V	MC	2
3	Ammeters	(0-10m) A	MC	2


4	Resistors	1k $\Omega$ 2.2 K $\Omega$ 470 $\Omega$	Carbon Composition	2 1 1
5	Bread board	-	-	1
6	Connecting wires	-	-	Required Number

**PRECAUTIONS:**

1. Initially keep the RPS output voltage knob in zero volt position.
2. Set the ammeter pointer to zero position.
3. Take the readings without parallax error.
4. Avoid loose connections.
5. Do not short-circuit the RPS output terminals.

**PROCEDURE:**

1. Connect the circuit as per the fig.
2. Adjust the output voltage of the regulated power supply to an appropriate value (Say 10V).
3. Note down the corresponding current ( $I_1$ ) through the input port, 1-1' and voltage ( $V_2$ ) across the output port, 2-2'.
4. Reduce the voltage to zero, disconnect the circuit and calculate  $Z_{11}$  and  $Z_{21}$  using the formulae,  $Z_{11}=V_1/I_1$  and  $Z_{21}=V_2/I_1$ .
5. Connect the circuit as per the fig .
6. Vary the R.P.S. output voltage to 5V, 10V and 15V
7. Reduce the voltage to zero, disconnect the circuit and calculate  $Z_{22}$  and  $Z_{12}$  using the formulae,  $Z_{22}=V_2/I_2$  and  $Z_{12}=V_1/I_2$

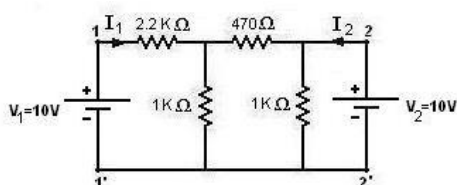**DETERMINATION OF Z PARAMETERS****GIVEN CIRCUIT:**

**Theoretical circuit diagrams:**

a) To find  $Z_{11}$  &  $Z_{21}$ :

**Practical circuit diagrams:**

a) To find  $Z_{11}$  &  $Z_{21}$ :

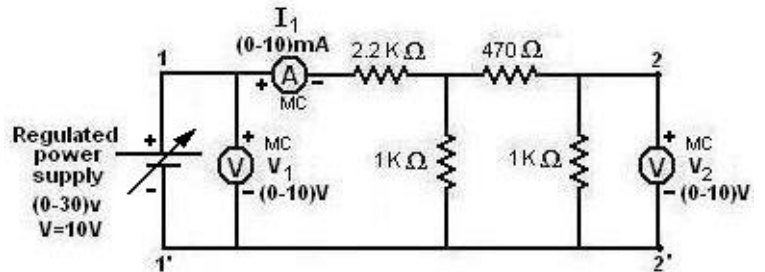


Fig.

**Tabular Column:**


S. No	$V_1$ (Volts)	$V_2$ (Volts)	$I_1$ (mA)	$Z_{11} = \frac{V_1}{I_1} \text{ k}\Omega$	$Z_{21} = \frac{V_2}{I_1} \text{ k}\Omega$

**Theoretical circuit diagrams:**

b) To find  $Z_{22}$  &  $Z_{12}$ :

**Practical circuit diagrams:**

b) To find  $Z_{22}$  &  $Z_{12}$ :

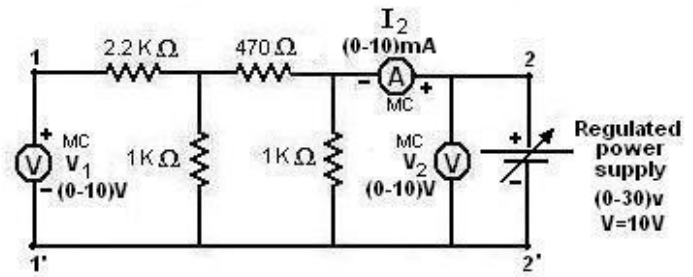

S. No	V <sub>1</sub> (volts)	V <sub>2</sub> (volts)	I <sub>2</sub> (mA)	$Z_{22} = \frac{V_2}{I_2} \text{ k}\Omega$	$Z_{12} = \frac{V_1}{I_2} \text{ k}\Omega$

**RESULT:**

Open circuited impedance parameters are determined and are compared with theoretical values.

S.No	Parameter	Theoretical Values	Practical Values
1	$Z_{11}$		
2	$Z_{12}$		
3	$Z_{21}$		
4	$Z_{22}$		

**CONCLUSIONS:**

1. Since  $Z_{12} = Z_{21}$  the given circuit is reciprocal.
2. Since  $Z_{11} = Z_{22}$  the given circuit is symmetrical.
3. There is a small deviation between theoretical and practical values because internal resistances of source and meters are not considered.

**EXPT NO:06****DATE:****DETERMINATION OF Y PARAMETERS****AIM:** To determine Short circuit admittance parameters (Y) of the given two port network.

**BRIEF THEORY :**In Y parameters of a two-port , the input & output currents  $I_1$  &  $I_2$  can be expressed in terms of input & output voltages  $V_1$  &  $V_2$  . Out of four variables (i.e  $I_1$ ,  $I_2$ ,  $V_1$ ,  $V_2$ )  $I_1$  &  $I_2$  are dependent variables whereas  $V_1$  &  $V_2$  are independent variables.

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \text{----- (1)}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \text{----- (2)}$$

Here  $Y_{11}$  &  $Y_{22}$  are the input & output driving point admittances while  $Y_{12}$  &  $Y_{21}$  are the reverse & forward transfer admittances.

**APPARATUS:**

S. No	Name of the apparatus	Range	Type	Quantity
1	Dual channel Regulated power supply	(0 – 30)V	-	1
2	Voltmeters	(0-10) V	MC	2
3	Ammeters	(0-10m) A	MC	2
4	Resistors	1k $\Omega$ 2.2 K $\Omega$ 470 $\Omega$	Carbon Composition	2 1 1
5	Bread board	-	-	1
6	Connecting wires	-	-	Required Number


**PRECAUTIONS:**

1. Initially keep the RPS output voltage knob in zero volt position.
2. Set the ammeter pointer to zero position.
3. Take the readings without parallax error.

4. Avoid loose connections.
5. Do not short-circuit the RPS output terminals.

**PROCEDURE:**

1. Connect the circuit as per the fig.
2. Vary the R.P.S. output voltage to 5V, 10V and 15V.
3. Note down the corresponding currents through the input port  $I_1$  and output port  $I_2$ .
4. Reduce the voltage to zero, disconnect the circuit and calculate  $Y_{11}$  and  $Y_{21}$  using the formulae,  $Y_{11}=I_1/V_1$  and  $Y_{21}=I_2/V_1$ .
5. Connect the circuit as per the fig.
6. Vary the R.P.S. output voltage to 5V, 10V and 15V..
7. Note down the corresponding currents through the input port  $I_1$  and output port  $I_2$ .
8. Reduce the voltage to zero, disconnect the circuit and calculate  $Y_{11}$  and  $Y_{21}$  using the formulae,  $Y_{12}=I_1/V_2$  and  $Y_{22}=I_2/V_2$ .

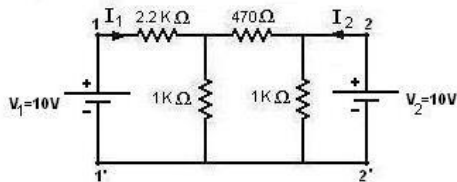**GIVEN CIRCUIT:**

Theoretical circuit diagrams:	Practical circuit diagrams:
A) <u>To find <math>Y_{11}</math> &amp; <math>Y_{21}</math>:</u>	B) <u>To find <math>Y_{11}</math> &amp; <math>Y_{21}</math>:</u>

**Tabular Column:**

S. No	V <sub>1</sub> (volts)	I <sub>2</sub> (mA)	I <sub>1</sub> (mA)	$Y_{11} = \frac{I_1}{V_1}$ (mho)	$y_{21} = \frac{I_2}{V_1}$ (mho)

Theoretical circuit diagrams:	Practical circuit diagrams:												
<p>b) <u>To find <math>y_{22}</math> &amp; <math>y_{12}</math>:</u></p>	<p>b) <u>To find <math>y_{22}</math> &amp; <math>y_{12}</math>:</u></p> <div style="text-align: center;"> </div> <table border="1" style="width: 100%; border-collapse: collapse; text-align: center; margin-top: 10px;"> <thead> <tr> <th>S. No</th> <th>V<sub>2</sub> (volts)</th> <th>I<sub>2</sub> (mA)</th> <th>I<sub>1</sub> (mA)</th> <th><math>y_{22} = \frac{I_2}{V_2}</math> (mho)</th> <th><math>Y_{12} = \frac{I_1}{V_2}</math> (mho)</th> </tr> </thead> <tbody> <tr> <td> </td> <td> </td> <td> </td> <td> </td> <td> </td> <td> </td> </tr> </tbody> </table>	S. No	V <sub>2</sub> (volts)	I <sub>2</sub> (mA)	I <sub>1</sub> (mA)	$y_{22} = \frac{I_2}{V_2}$ (mho)	$Y_{12} = \frac{I_1}{V_2}$ (mho)						
S. No	V <sub>2</sub> (volts)	I <sub>2</sub> (mA)	I <sub>1</sub> (mA)	$y_{22} = \frac{I_2}{V_2}$ (mho)	$Y_{12} = \frac{I_1}{V_2}$ (mho)								

**RESULT:**

Open circuited impedance and short circuit admittance parameters are determined and are compared with theoretical values.

S.No	Parameter	Theoretical Values	Practical Values

1	$Y_{11}$		
2	$Y_{12}$		
3	$Y_{21}$		
4	$Y_{22}$		

**CONCLUSIONS:**

4. Since  $Y_{12} = Y_{21}$  the given circuit is reciprocal.
5. Since  $Y_{11} = Y_{22}$  the given circuit is symmetrical.
6. There is a small deviation between theoretical and practical values because internal resistances of source and meters are not considered.

Expt. No.: 07

Date:

### DETERMINATION OF ABCD PARAMETERS

**AIM:** To determine transmission parameters (ABCD) of the given two port network.

**BRIEF THEORY:** ABCD parameters are widely used in analysis of power transmission engineering where they are termed as “Circuit Parameters”. ABCD parameters are also known as “Transmission Parameters”. In these parameters, the voltage & current at the sending end terminals can be expressed in terms of voltage & current at the receiving end. Thus,

$$V_1 = AV_2 + B(-I_2)$$


$$I_1 = CV_2 + D(-I_2)$$

Here “A” is called reverse voltage ratio, “B” is called transfer impedance “C” is called transfer admittance & “D” is called reverse current ratio.

**APPARATUS:**

S. No	Name of the apparatus	Range	Type	Quantity
1	Dual channel Regulated power supply	(0 – 30)V	-	1
2	Voltmeters	(0-10) V	MC	2
3	Ammeters	(0-10m) A	MC	2
4	Resistors	1k $\Omega$ 2.2 K $\Omega$ 470 $\Omega$	Carbon Composition	2 1 1
5	Bread board	-	-	1
6	Connecting wires	-	-	Required Number

**Given Circuit**

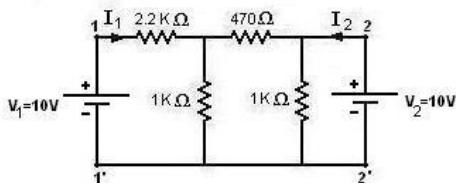

**Theoretical circuit diagrams:**

b) To find B&D:

**Practical circuit diagrams:**

b) To find B&D:

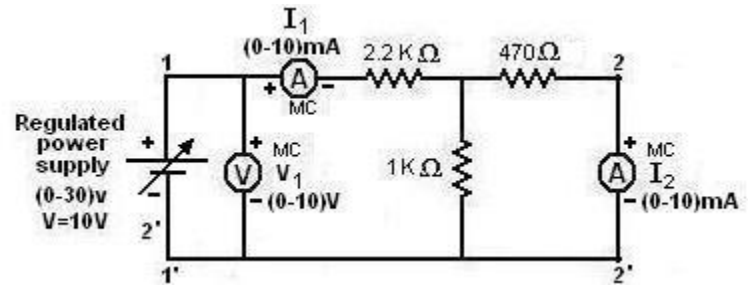


Fig.

**Tabular Column:**

S. No	V <sub>1</sub> (volts)	I <sub>2</sub> (mA)	I <sub>1</sub> (mA)	$B = \frac{V_1}{I_2}$ (kΩ)	$D = \frac{I_1}{I_2}$

**Theoretical circuit diagrams:**

b) To find A&C:

**Practical circuit diagrams:**

b) To find A & C:

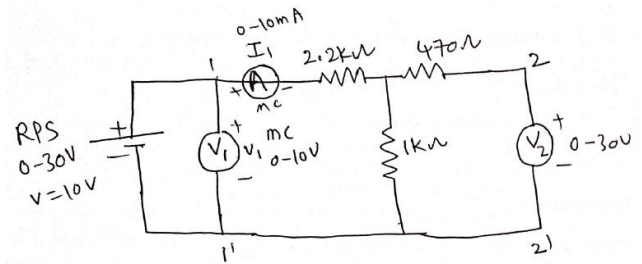


Fig.

**Tabular Column:**

S. No	V <sub>1</sub> (Volts)	V <sub>2</sub> (Volts)	I <sub>1</sub> (mA)	A = $\frac{V_1}{V_2}$	C = $\frac{I_1}{V_2}$

**PROCEDURE:**

1. Connect the circuit as per the fig.
2. Adjust the output voltage of the regulated power supply to an appropriate value (Say 10V).
3. Note down the corresponding current ( $I_1$ ) through the input port, 1-1<sup>1</sup> and voltage ( $V_2$ ) across the output port, 2-2<sup>1</sup>.
4. Reduce the voltage to zero, disconnect the circuit and calculate A and C using the formulae,  $A=v_1/v_2$  and  $C=I_1/V_2$ .
5. Connect the circuit as per the fig.
6. Vary the R.P.S. output voltage to 5V, 10V and 15V
7. Note down the corresponding current ( $I_2$ ) through the output port 2-2<sup>1</sup> and voltages ( $V_1$  &  $V_2$ ) across the input port 1-1<sup>1</sup> & output port 2-2<sup>1</sup> resp'y.
8. Reduce the voltage to zero, disconnect the circuit and calculate B and D using the formulae,  $B=V_1/I_2$  and  $D=I_1/I_2$
9. Connect the circuit as per the fig.
10. Vary the R.P.S. output voltage to 5V, 10V and 15V.
11. Note down the corresponding currents through the input port  $I_1$  and output port  $I_2$ .
12. Reduce the voltage to zero, disconnect the circuit and calculate  $h_{11}$  and  $h_{21}$  using the formulae,  $h_{11}=V_1/I_1$  and  $h_{21}=I_2/I_1$ .
13. Connect the circuit as per the fig.
14. Vary the R.P.S. output voltage to 5V, 10V and 15V..
15. Note down the corresponding currents through the input port  $I_1$  and output port  $I_2$ .
16. Reduce the voltage to zero, disconnect the circuit and calculate  $h_{22}$  and  $h_{12}$  using the formulae,  $h_{22}=I_2/V_2$  and  $h_{12}=V_1/V_2$ .

**PRECAUTIONS:**

1. Initially keep the RPS output voltage knob in zero volt position.
2. Set the ammeter pointer to zero position.
3. Take the readings without parallax error.
4. Avoid loose connections.
5. Do not short-circuit the RPS output terminals.

**RESULT:**

Transmission parameters are determined and are compared with theoretical values.

S.No	Parameter	Theoretical Values	Practical Values
1	A		
2	B		
3	C		
4	D		

**CONCLUSIONS:**

Expt. No.: 08

Date:

**DETERMINATION OF H PARAMETERS**

**AIM:** To determine hybrid parameters (h) of the given two port network.

**BRIEF THEORY:** In 'h' parameters of a two port network, voltage of the input port and the current of the output port are expressed in terms of the current of the input port and the voltage of the output port. Due to this reason, these parameters are called as 'hybrid' parameters, i.e. out of four variables (i.e.  $V_1$ ,  $V_2$ ,  $I_1$ ,  $I_2$ )  $V_1$ ,  $I_2$  are dependent variables.

Thus,

$$V_1 = h_{11}I_1 + h_{12}V_2 \text{-----(1)}$$


$$I_2 = h_{21}I_1 + h_{22}V_2 \text{-----(2)}$$

$H_{11}$  and  $H_{22}$  are input impedance and output admittance.

$H_{21}$  and  $H_{12}$  are forward current gain and reverse voltage gain.

**APPARATUS:**

S. No	Name of the apparatus	Range	Type	Quantity
1	Dual channel Regulated power supply	(0 – 30)V	-	1
2	Voltmeters	(0-10) V	MC	2
3	Ammeters	(0-10m) A	MC	2
4	Resistors	1k $\Omega$ 2.2 K $\Omega$ 470 $\Omega$	Carbon Composition	2 1 1
5	Bread board	-	-	1
6	Connecting wires	-	-	Required Number

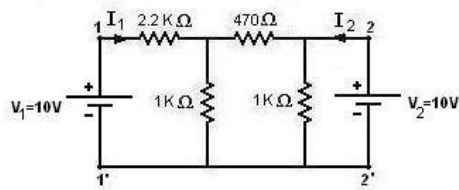

**Theoretical circuit diagrams:**

a) To find  $h_{11}$  &  $h_{21}$ :

$$\therefore h_{11} = \frac{V_1}{I_1} =$$

$$\therefore h_{21} = \frac{I_2}{I_1} =$$

**Practical circuit diagrams:**

a) To find  $h_{11}$  &  $h_{21}$

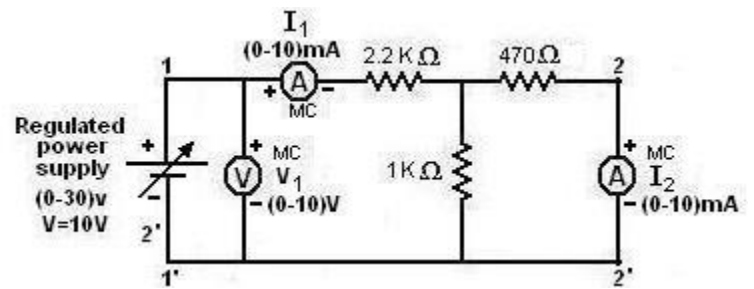


Fig.

**Tabular Column:**

S. No	$V_1$ (volts)	$I_2$ (mA)	$I_1$ (mA)	$h_{11} = \frac{V_1}{I_1}$ (kΩ)	$h_{21} = \frac{I_2}{I_1}$

)To find  $h_{12}$  &  $h_{22}$ :

$$h_{12} = \frac{V_1}{V_2}$$

$$h_{22} = \frac{I_2}{V_2}$$

) To find  $h_{12}$  &  $h_{22}$ :

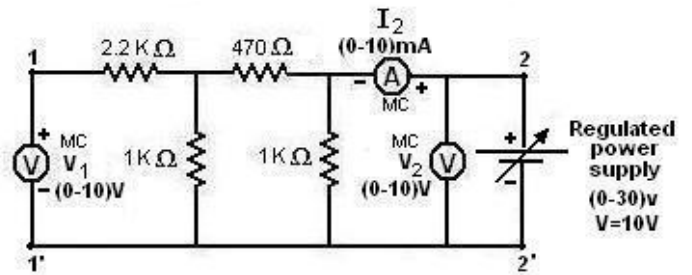


Fig. (3.4)

S. No	$V_1$ (volts)	$V_2$ (volts)	$I_2$ (mA)	$h_{12} = \frac{V_1}{V_2}$	$h_{22} = \frac{I_2}{V_2}$

**PROCEDURE:**

1. Connect the circuit as per the fig.
2. Vary the R.P.S. output voltage to 5V, 10V and 15V.
3. Note down the corresponding currents through the input port  $I_1$  and output port  $I_2$ .
4. Reduce the voltage to zero, disconnect the circuit and calculate  $h_{11}$  and  $h_{21}$  using the formulae,  $h_{11}=V_1/I_1$  and  $h_{21}=I_2/I_1$ .
5. Connect the circuit as per the fig.
6. Vary the R.P.S. output voltage to 5V, 10V and 15V..
7. Note down the corresponding currents through the input port  $I_1$  and output port  $I_2$ .
8. Reduce the voltage to zero, disconnect the circuit and calculate  $h_{22}$  and  $h_{12}$  using the formulae,  $h_{22}=I_2/V_2$  and  $h_{12}=V_1/V_2$ .

**PRECAUTIONS:**

1. Initially keep the RPS output voltage knob in zero volt position.
2. Set the ammeter pointer to zero position.
3. Take the readings without parallax error.
4. Avoid loose connections.
5. Do not short-circuit the RPS output terminals.

**RESULT:**

Hybrid parameters are determined and are compared with theoretical values.

S.No	Parameter	Theoretical Values	Practical Values
1	$h_{11}$		
2	$h_{12}$		
3	$h_{21}$		

4	$h_{22}$		
---	----------	--	--

**CONCLUSIONS:**

1. Since  $Z_{12} = Z_{21}$  and  $Y_{12} = Y_{21}$  the given circuit is reciprocal.
2. Since  $Z_{11} = Z_{22}$  and  $Y_{11} = Y_{22}$  the given circuit is symmetrical.
3. There is a small deviation between theoretical and practical values because internal resistances of source and meters are not considered.
- 4.

Expt. No.: 09

Date:

**DETERMINATION OF COEFFICIENT OF COUPLING****AIM:** To determine the coefficient of coupling of the given 1- $\phi$  transformer.**APPARATUS:**

S. No	Name of the apparatus	Range	Type	Quantity
1	Single phase transformer	230V / 115V, 2KVA	-	1No
2	1- $\phi$ auto transformer	230V / 0-270V, 10A, 2.7 KVA	-	1No
3	Ammeter	(0-2) A	MI	1 No
4	Voltmeter	(0-600) / (0-300) V	MI	1No
5	Wattmeter	0-150 / 300 / 600V 2.5 / 5A, LPF	DM	1No
6	3- $\phi$ auto transformer	415 / 0-470V, 10A, 4.7 KVA	-	1No
7	Connecting wires	-	-	Required number

**PROCEDURE:**

1. Connect the circuit as per the fig.
2. Apply 230V across the primary winding by varying the knob of autotransformer slowly.
3. Note down the corresponding voltmeter, ammeter, and wattmeter readings.
4. Calculate the self-inductance,  $L_1$  of the primary coil with the help of above readings.
5. Disconnect the circuit and connect the circuit as per the fig.
6. Apply 115V across the secondary winding by varying the knob of autotransformer slowly.
7. Note down the corresponding voltmeter, ammeter, and wattmeter readings.
8. Calculate the self-inductance,  $L_2$  of the secondary coil with the help of above readings.
9. Disconnect the circuit and connect the circuit as per the fig .
10. Apply 345V across the cumulatively coupled windings by varying the knob of 3- $\phi$  autotransformer slowly.
11. Note down the corresponding voltmeter, ammeter, and wattmeter readings.
12. Calculate the equivalent inductance,  $L_A$  of the windings with the help of above readings.
13. Disconnect the circuit and connect the circuit as per the fig .


14. Apply 115V across the differentially coupled windings by varying the knob of 1- $\phi$  autotransformer slowly.
15. Note down the corresponding voltmeter, ammeter, and wattmeter readings and disconnect the circuit.
16. Calculate the equivalent inductance,  $L_B$  of the windings with the help of above readings.
17. Calculate Mutual inductance  $M$ , and coefficient of coupling  $K$ , using the values of  $L_1, L_2, L_A, L_B$ .

**PRECAUTIONS:**

1. Ensure the minimum position of autotransformer during power on and off.
2. Set the ammeter pointer at zero position.
3. Take the readings with out parallax error.
4. Avoid loose connections.

**CIRCUIT DIAGRAMS:**

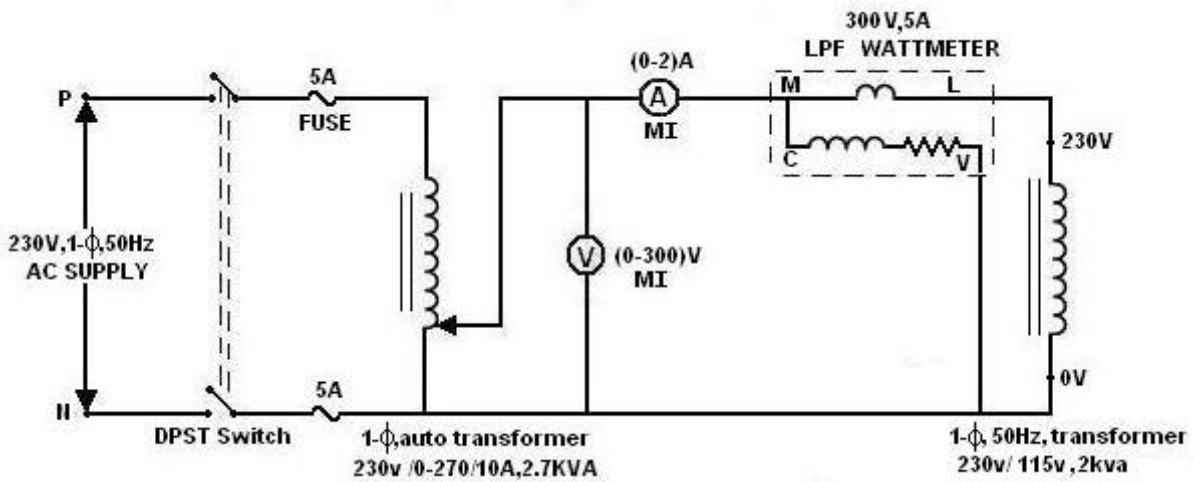
a) To determine the self inductance of coil 1:



Tabular column:

S.No	$V_1$ (Volts)	$I_1$ (amp)	$W_1$ (Watt)	$Z_1 = \frac{V_1}{I_1} \Omega$	$R_1 = \frac{W_1}{I_1^2} \Omega$	$X_{L_1} = \sqrt{Z_1^2 - R_1^2} \Omega$	$L_1 = \frac{X_{L_1}}{2\pi f} H$

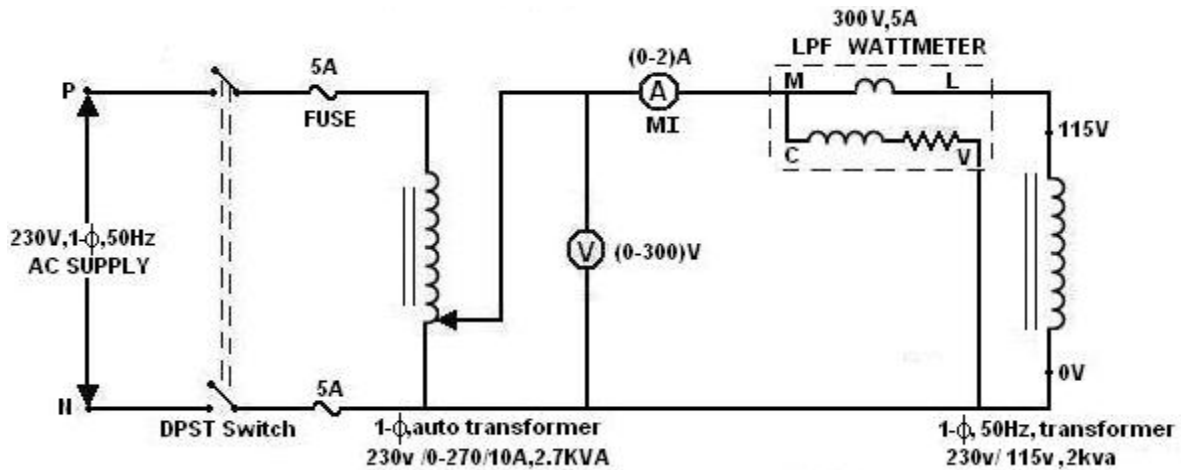b) To determine the self inductance of coil 2:



Tabular column:


S.No	V <sub>2</sub> (Volts)	I <sub>2</sub> (amp)	W <sub>2</sub> (Watt)				

**RESULT:**


The coefficient of coupling K is determined for the given 1-φ transformer.

**CONCLUSION:**

The coefficient of coupling, K of the given 1-φ iron cored transformer is less than unity.

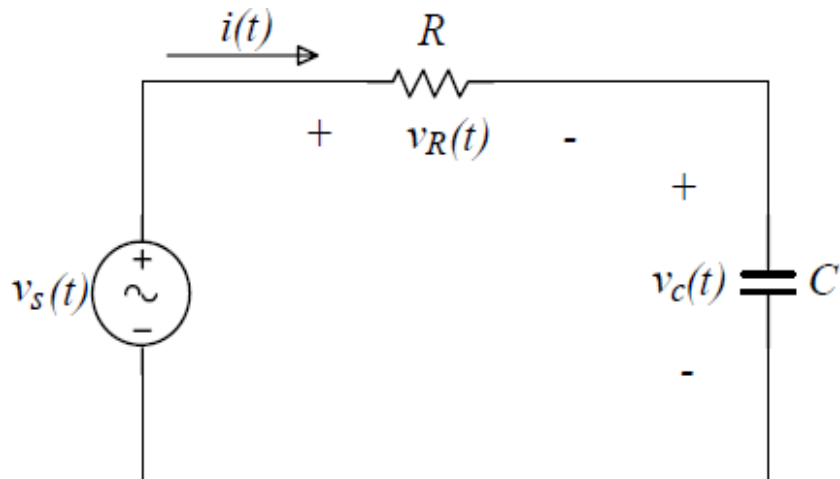**CIRCUIT DIAGRAM :**

**Figure 1. Series RC circuit driven by a sinusoidal forcing function**

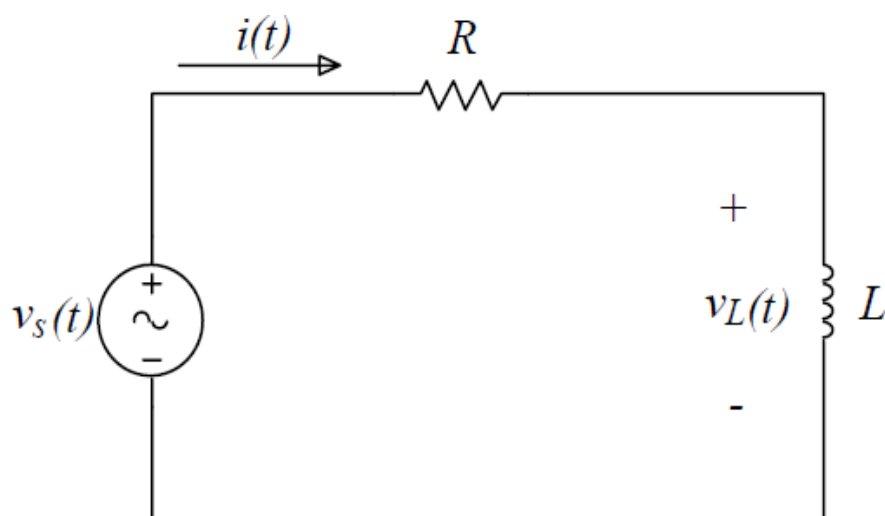

**Figure 2: Series RL circuit driven by a sinusoidal forcing function**

Expt. No.: 10

Date:

<b>Exp. No.:</b>	<b>Response Analysis of R, RL and RLC circuits with sinusoidal excitations</b>
<b>Date:</b>	

**Aim:**


To determine the sinusoidal response of series RL and RC circuit with sinusoidal excitations

**Apparatus:**

S. No.	Name of the Equipment	Range	Type	Quantity
1	Function generator			1
2	Bread Board			1
3	Resistor			1
4	Inductor			1
5	Capacitor			1
6	Connecting Wires			--

**PROCEDURE :**

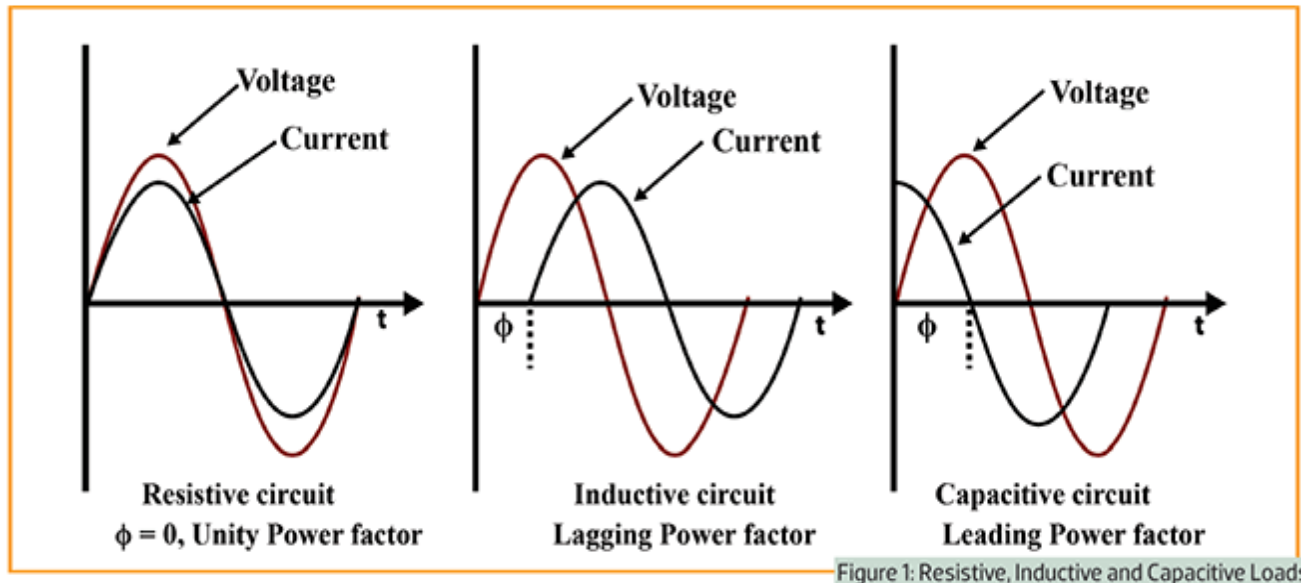- (1) Connect the apparatus as per the circuit diagram.
- (2) Apply a sinusoidal voltage using function generator.
- (3) Note down current with different frequencies
- (4) Switch off the supply and disconnect the circuit



**Result:**


**SIMULATION EXPERIENTS**

Exp. No.: 11

Date:

**SIMULATION OF D.C. CIRCUIT****AIM:** To Simulate the DC Circuit for determining the Thevenin's equivalent circuit using PSPICE.**SOFTWARE REQUIRED:** PSPICE – Personal Computer Simulated Program with Integrated Circuit Emphasis.**DATA REQUIRED FOR DRAWING CIRCUIT DIAGRAM:**

A DC Circuit is as shown in the figure. It Consists of Voltage Source whose Value is **10V**; the Current source has the Value of **2A**. It has the resistance values as **5Ω, 10Ω, 20Ω, 40Ω, and 10Ω** respectively. Use PSPICE to plot and calculate the Thevenin's Equivalent Circuit across thenodes **2** and **4**. Obtain the transfer function between the two nodes **2** and **4**.

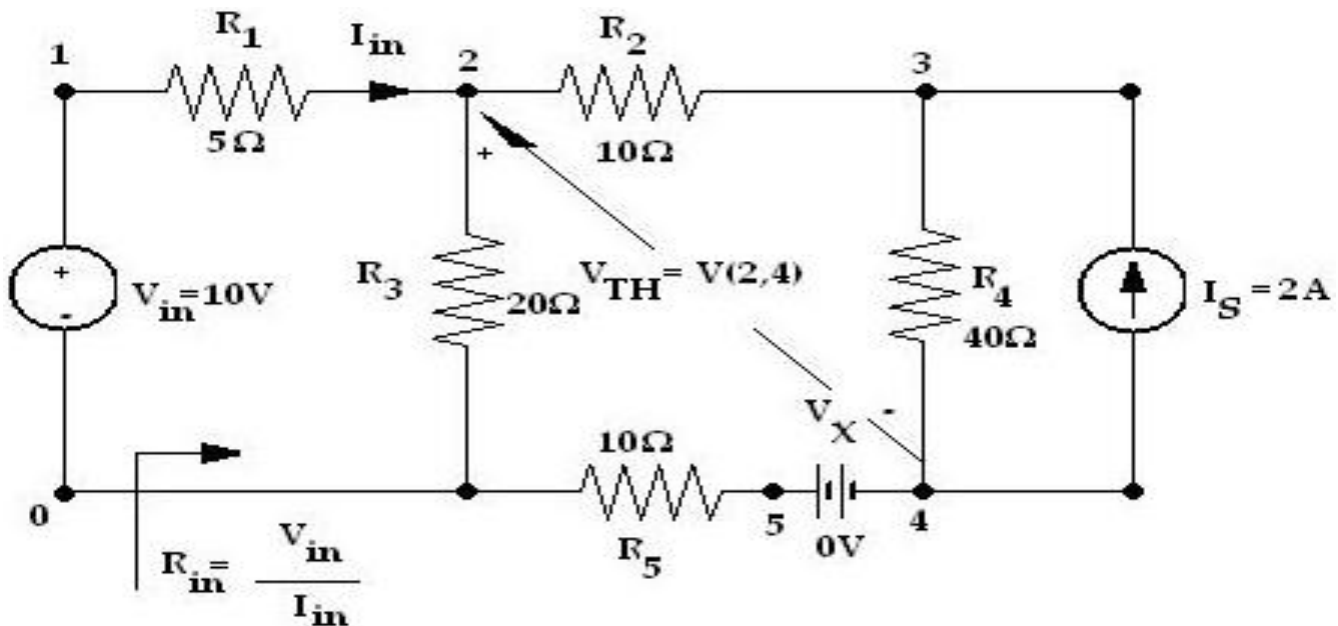**CIRCUIT DIAGRAM:****PROCEDURE:**

1. Open PSPICE A/D windows
2. Create a new circuit file
3. Enter the program representing the nodal interconnections of various components
4. Run the program
5. Observe the response through all the elements in the output file
6. Observe the voltage, current graph of any in probe window

**PROGRAM****THEVENINS THEOREM:**

```
VIN1 0 dc 10V
IS 4 3 2A
VX 4 5 dc 0V
R11 2 5
R2 2 3 10
R32 0 20
R4 3 4 40
R55 0 10
.TF V(2,4) VIN
.END
```

**THEORETICAL CALCULATIONS**

**RESULT:****VIVA QUESTIONS:**

1. What is  $V_{th}$  or Thevenin's voltage?
2. How equivalent impedance is calculated in Thevenin Theorem?
3. What are internal resistance of an ideal voltage source and an ideal current source?
4. State Thevenin's theorem?
5. What are active elements and passive elements?
6. What are non linear elements and give examples?
7. Can you find maximum power transferred to the load by using Thevenins theorem?
8. Write the formulae to convert a current source into voltage source?
9. Write the formulae to convert a voltage source into current source?
10. Define KVL and KCL?

Exp. No.:12


Date:

## SIMULATION OF AC CIRCUITS

**AIM:** To calculate the response for the ac circuits.

**SOFTWARE REQUIRED:** PSPICE – Personal Computer Simulated Program with Integrated Circuit Emphasis.

**Circuit diagram:**

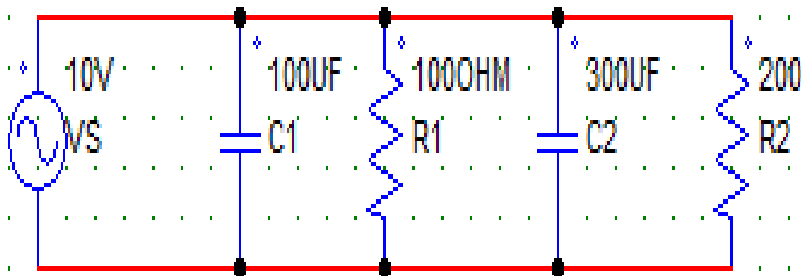

**Program:**

```
VS 1 0 AC 10V
```

```
C1 1 0 100U
```

```
R1 1 0 100
```

```
C2 1 0 300U
```

```
R2 1 0 200
```

```
.AC LIN 1 50 100
```

```
.PRINT AC IM(VS) IP(VS) IM(C1) IP(C1)
```

```
.END
```

**Output:**

**Result:**