

**Electrical Circuit  
Analysis  
(20A02301T)**

**By  
Dr.A.Hema Sekhar  
Professor in EEE  
VEMU Institute of  
Technology**

# SYLLABUS

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY ANANTAPUR**  
**(Established by Govt. of A.P., ACT No.30 of 2008)**  
**ANANTHAPURAMU – 515 002 (A.P) INDIA**

ELECTRICAL AND ELECTRONICS ENGINEERING

ELECTRICAL CIRCUIT ANALYSIS

L T P C

Course Code  
20A02301T

3 0 0 3

UNIT - I Locus Diagrams & Resonance

8 Hrs

Series R-L, R-C, R-L-C and Parallel Combination with Variation of Various Parameters -Resonance-Series, Parallel Circuits, Frequency Response, Concept of Bandwidth and Q Factor.

UNIT - II Two Port Networks

9 Hrs

Two Port Network Parameters – Impedance – Admittance - Transmission and Hybrid Parameters and their Relations - Concept of Transformed Network - Two Port Network Parameters Using Transformed Variables.

UNIT - III Transient Analysis 12 Hrs

D.C Transient Analysis: Transient Response of R-L, R-C, R-L-C Series Circuits for D.C Excitation - Initial Conditions in network - Initial Conditions in elements - Solution Method Using Differential Equation and Laplace Transforms - Response of R-L & R-C Networks to Pulse Excitation. A.C Transient Analysis: Transient Response of R-L, R-C, R-L-C Series Circuits for Sinusoidal Excitations - Solution Method Using Differential Equations and Laplace Transforms.

# SYLLABUS

## UNIT - IV Fourier Transforms

10 Hrs

Fourier Theorem - Trigonometric Form and Exponential Form of Fourier series – Conditions of Symmetry - Line Spectra and Phase Angle Spectra - Analysis of Electrical Circuits to Non Sinusoidal Periodic Waveforms. Fourier Integrals and Fourier Transforms – Properties of Fourier Transforms and Application to Electrical Circuits.

## UNIT - V Filters

9

Hrs

Filters – Low Pass – High Pass, Band Pass and Band Stop– RC, RL filters– derived filters and composite filters design – Attenuators – Principle of Equalizers – Series and Shunt Equalizers – L Type - T type and Bridged – T and Lattice Equalizers.

### Textbooks:

1. William Hayt, Jack E. Kemmerly and Jamie Phillips, "Engineering Circuit Analysis", McGraw Hill, 9th Edition, 2019.
2. A. Chakrabarti, "Circuit Theory: Analysis & Synthesis", DhanpatRai& Sons, 2008. Reference Books:
  1. M.E. Van Valkenberg, "Network Analysis", 3rd Edition, Prentice Hall (India), 1980.
  2. V. Del Toro, "Electrical Engineering Fundamentals", Prentice Hall International, 2009.
  3. Charles K. Alexander and Matthew. N. O. Sadiku, "Fundamentals of Electric Circuits" McGraw Hill, 5th Edition, 2013.
  4. MahamoodNahvi and Joseph Edminister, "Electric Circuits" Schaum's Series, 6th Edition, 2013.
  5. John Bird, Routledge, "Electrical Circuit Theory and Technology", Taylor & Francis, 5th Edition, 2014.

# Unit-1:Locus Diagrams & Resonance

Def of Locus diagram:

"It is defined as the Locus of the current obtained for various values of the variable element."


classification

Locus diagrams are classified into two types

- ① series R-L, R-C and R-L-C circuits.
- ② Parallel combination of circuits.

# Unit-1: Locus Diagrams & Resonance contd...

Locus diagram of R-L circuit :-

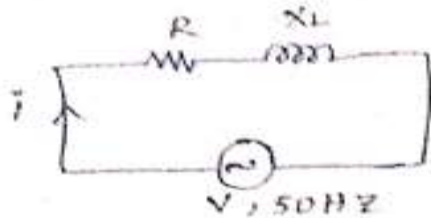



According to KVL

$$V = I(R + jX_L)$$


$$V = IZ \quad , \quad Z = R + jX_L$$

$$I = \frac{V}{Z} \longrightarrow (1)$$

Impedance diagram

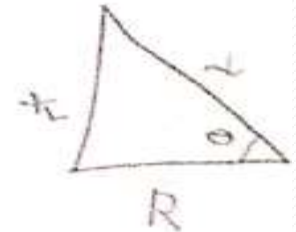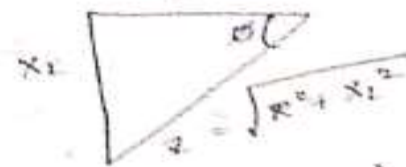

Now, phasor diagram for R-L circuit is

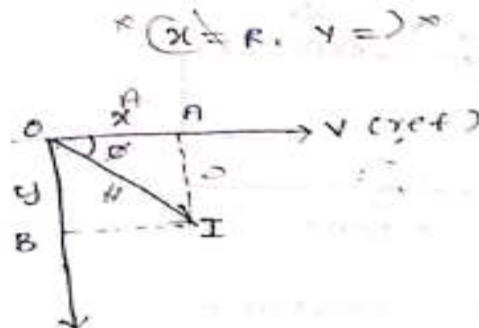

# Unit-1:Locus Diagrams & Resonance contd...

From the phasor diagram

$$\cos \phi = \frac{x}{I}$$

$$x = I \cos \phi \longrightarrow (2)$$

$$\sin \phi = \frac{OB}{I} = \frac{y}{-I}$$

$$y = -I \sin \phi \longrightarrow (3)$$

$$x^2 + y^2 = I^2 \cos^2 \phi + I^2 \sin^2 \phi$$

$$x^2 + y^2 = I^2 (\cos^2 \phi + \sin^2 \phi)$$

# Unit-1: Locus Diagrams & Resonance contd...

$$x^2 + y^2 = I^2$$


$$x^2 + y^2 = \left(\frac{V}{Z}\right)^2$$

$$x^2 + y^2 = \frac{V^2}{Z^2}$$

$$x^2 + y^2 = \frac{V^2}{(\sqrt{R^2 + X_L^2})^2}$$

$$\therefore x^2 + y^2 = \frac{V^2}{R^2 + X_L^2} \longrightarrow (4)$$

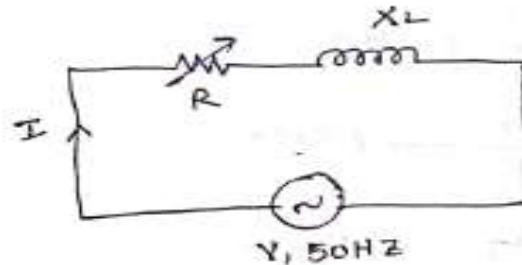Case (i) :- Variable  $R$ , constant  $X_L$



# Unit-1:Locus Diagrams & Resonance contd...

Here  $X_L$  is constant

$$y = -I \sin \phi$$

$$= -\frac{V}{Z} \times \frac{X_L}{Z}$$

$$= -\frac{V X_L}{R^2 + X_L^2}$$

$$y = -X_L \times \frac{V}{R^2 + X_L^2} \longrightarrow (5)$$

$$\frac{V}{R^2 + X_L^2} = \frac{-y}{X_L} \longrightarrow (6)$$

Substitute Eqn (6) in Eqn (4)

# Unit-1:Locus Diagrams & Resonance contd...

$$x^2 + y^2 = \frac{V}{R^2 + X_L^2} \cdot y$$

$$x^2 + y^2 = \frac{V}{X_L} \cdot \frac{y}{2}$$

$$x^2 + y^2 + 2y \cdot \frac{V}{2X_L} + \left(\frac{V}{2X_L}\right)^2 - \left(\frac{V}{2X_L}\right)^2 = 0$$

$$x^2 + \left(y + \frac{V}{2X_L}\right)^2 = \left(\frac{V}{2X_L}\right)^2$$

$$\therefore x^2 + \left(y + \frac{V}{2X_L}\right)^2 = \left(\frac{V}{2X_L}\right)^2 \longrightarrow (7)$$

Now we know the circle equation

$$(x - x_1)^2 + (y - y_1)^2 = r^2 \longrightarrow (8)$$

# Unit-1: Locus Diagrams & Resonance contd...

comparing eqn's (7) & (8), we get,

$$x_1 = 0,$$

$$y_1 = \frac{-V}{2X_L}$$

at resonance  $\gamma = \frac{V}{2X_L}$

$$\therefore \text{Centre} = (x_1, y_1) = \left(0, \frac{-V}{2X_L}\right)$$

$$\text{radius } (\gamma) = \frac{V}{2X_L}$$

Construction of locus diagram :-

$$\cos \phi = \frac{R}{Z} \quad \text{Eq. (1)} \quad I = \frac{V}{Z} \quad \rightarrow \quad I = \frac{V}{\sqrt{R^2 + X_L^2}}$$


Suppose if  $\phi = 30^\circ$  then  $\cos 30^\circ = 0.866$

$\phi = 45^\circ$  then  $\cos 45^\circ = 0.707$

$\phi = 60^\circ$  then  $\cos \phi = 0.5$

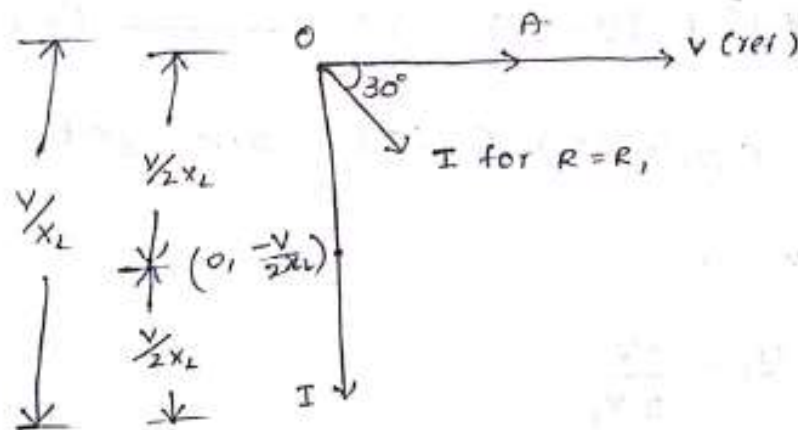
# Unit-1: Locus Diagrams & Resonance contd...

If  $\cos 30^\circ = 0.866$  and compared due to other angle it is high value and we know that  $R$  is directly proportional to  $\cos \phi$  and  $R$  value is high then if we put high value of  $R$  in current eqn then the magnitude of current is less. that means at  $30^\circ$  magnitude of current is less.


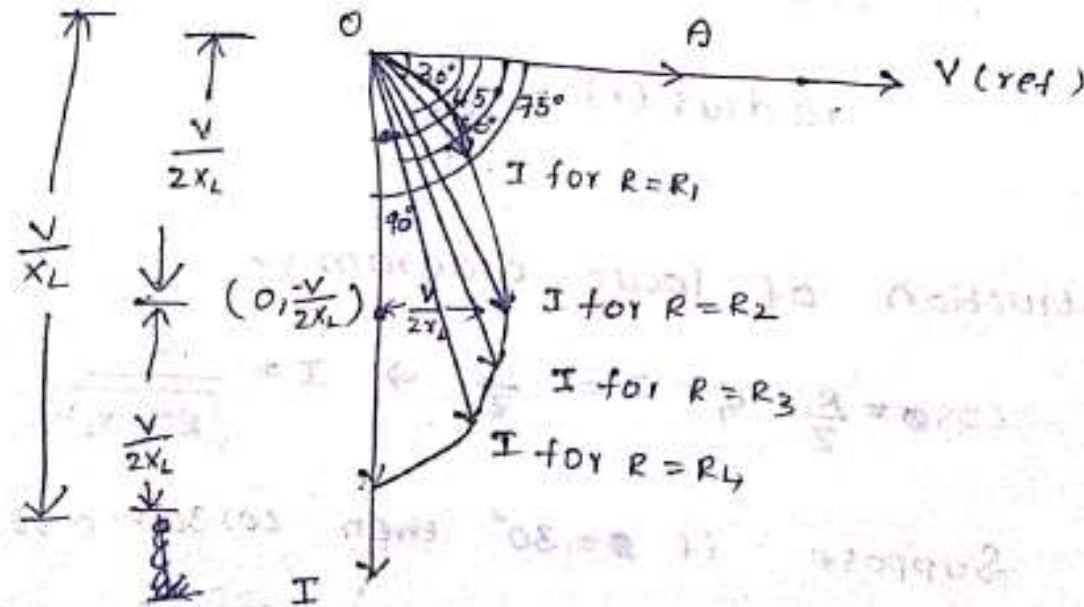
# Unit-1: Locus Diagrams & Resonance


If angle increases  $R'$  value decreases then current values increases.



# Unit-2: Two Port Networks
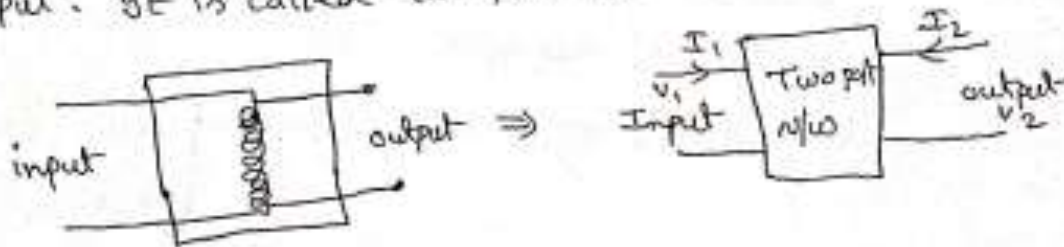
## Two port n/w

It is the rectangular box represents a network, consists of two pairs of network [Four terminals] where one pair of terminals can be designated as input, the other pair being output. It is called two port n/w.



## Types of two port parameters

- In Two port n/w, four variables are  $V_1, I_1, V_2, I_2$
- out of four variables, two variables are dependent and other two variables are independent variables.
- These dependent & independent variables are depends on the type of Parameter.

# Unit-2: Two Port Networks contd...

① z-parameters (or) open ckt-parameters:

z-parameters are represented as

$$V_1 = z_{11}I_1 + z_{12}I_2 \quad (1)$$

$$V_2 = z_{21}I_1 + z_{22}I_2 \quad (2)$$




From the above equations

dependent variables:  $V_1$  &  $V_2$

Independent variables:  $I_1$  &  $I_2$

From eq (1) & (2) z-parameters are  $\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$

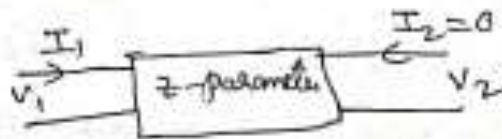cases: To find  $z_{11}$  &  $z_{21}$  by open cktng the output port i.e.  $I_2 = 0$ .



# Unit-2: Two Port Networks contd...

put  $I_2 = 0$  in eq (1) & (2)

From eq (1)  $V_1 = z_{11} I_1$


$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \rightarrow \text{Driving point Input Impedance}$$

From eq (2)

$$V_2 = z_{21} I_1$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \rightarrow \text{Forward transfer Impedance}$$

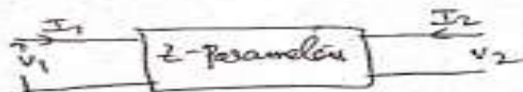Case (2): To find  $z_{12}$  &  $z_{22}$  by open circuiting port 1  
i.e.  $I_1 = 0$ .



Put  $I_1 = 0$  in eq (1) & (2)

From eq (1),  $V_1 = z_{12} I_2$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \rightarrow \text{Reverse transfer Impedance}$$

From eq (2)

$$V_2 = z_{22} I_2$$


$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \rightarrow \text{Driving point output Impedance}$$

# Unit-2: Two Port Networks contd...

## Problems
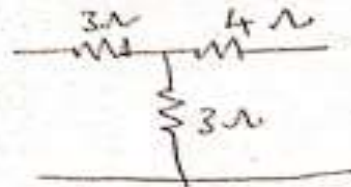
### Z-Parameters (Problem)

- ① Find Z-parameters for the following circ.



Sol

### Z-Parameters

$$V_1 = z_{11} I_1 + z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = z_{21} I_1 + z_{22} I_2 \quad \text{--- (2)}$$

Case (1) To find  $z_{11}$  &  $z_{21}$ , put  $I_2 = 0$   $\left[ z_{11} = \frac{V_1}{I_1}, z_{21} = \frac{V_2}{I_1} \right]$

Apply KVL for loop 1


$$V_1 - 3I_1 - 3I_1 - 3I_2 = 0$$

$$\text{Put } I_2 = 0$$

$$V_1 - 6I_1 = 0$$

$$V_1 = 6I_1$$
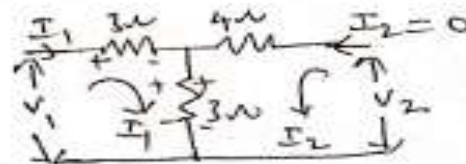
$$\boxed{\frac{V_1}{I_1} = 6 \Omega = z_{11}}$$



# Unit-2: Two Port Networks contd...

Apply KVL for loop 2

$$V_2 - 4I_2 - 3I_2 - 3I_1 = 0$$

$$\text{put } I_1 = 0$$

$$V_2 - 3I_2 = 0$$

$$V_2 = 3I_2$$

$$\boxed{\frac{V_2}{I_2} = z_{21} = 3 \Omega}$$

Case (2): To obtain  $z_{12}$  &  $z_{22}$ , put  $I_1 = 0$

$$z_{12} = \frac{V_1}{I_2}, \quad z_{22} = \frac{V_2}{I_2}$$

apply KVL for loop 1


$$V_1 - 3I_1 - 3I_1 - 3I_2 = 0$$

$$\text{put } I_1 = 0$$

$$V_1 - 3I_2 = 0$$

$$V_1 = 3I_2$$
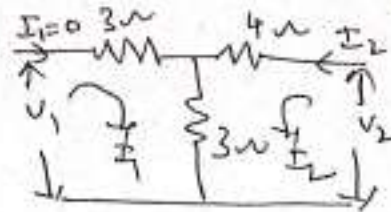
$$\boxed{\frac{V_1}{I_2} = z_{12} = 3 \Omega}$$



# Unit-2: Two Port Networks contd...

apply KVL for loop 2

$$V_2 - 4I_2 - 3I_2 - 3I_2 = 0$$

$$\text{put } I_1 = 0$$

$$V_2 - 7I_2 = 0$$

$$V_2 = 7I_2$$

$$\boxed{\frac{V_2}{I_2} = Z_{22} = 7 \Omega}$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 6 & 3 \\ 3 & 7 \end{bmatrix}$$


### Introduction

1. Steady state :

A circuit having voltage source or current source is said to be steady state if voltage and currents doesn't change with respect to time.

Ex:  $t = 2 \text{ sec}$  ,  $V = 10 \text{ V}$  ,  $I = 2 \text{ A}$

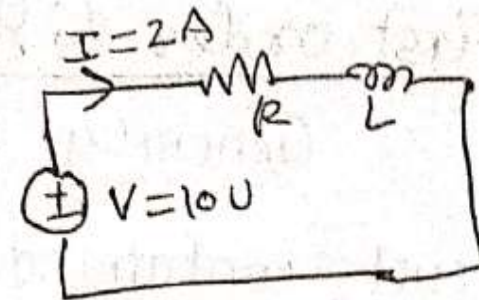$t = 5 \text{ sec}$  ,  $V = 10 \text{ V}$  ,  $I = 2 \text{ A}$



# III. TRANSIENTS

## Introduction

2. Transient state:


A circuit having voltage source, current source, circuit parameters like  $R, L$  &  $C$ . Now either change in voltage or current source or any one of the circuit parameters, then voltage and currents are changed from one state to another state is called transient state.

(OR)

The behaviour of voltage and currents when it is changed from one steady state to another steady state is called transient state.

Ex:  $t = 2 \text{ sec}$ ,  $V = 10 \text{ V}$ ,  $I = 2 \text{ A}$

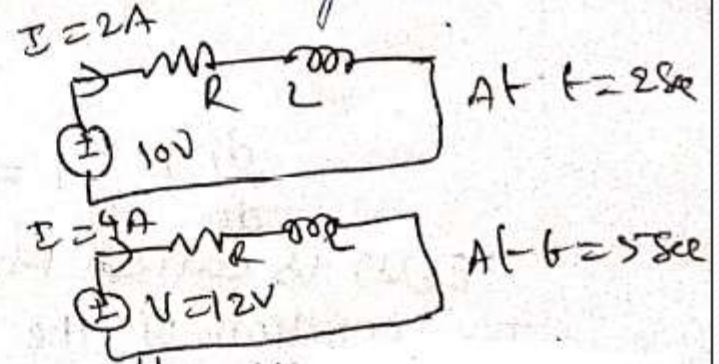$t = 5 \text{ sec}$ ,  $V = 12 \text{ V}$ ,  $I = 4 \text{ A}$



### 3. Transient time :

The time required for changing the voltage and currents from one state to another state is called Transient time.

### 4. Natural Response :

The circuit having circuit parameters like  $R, L, C$  with independent current and voltage sources, the response of output depends on the nature of the circuit, then the response is called natural response.

### 5 Transient Response:


The circuit having circuit parameters like  $R, L, C$  with independent voltage and current sources, then the energy storing elements ( $L$  &  $C$ ) which delivers energy to the resistors, the response or o/p change with time and get saturated.

### 6 Forced Response:

The circuits having circuit parameters like  $R, L, C$  with dependent voltage and current sources, the response or output depends on the sources, then it is called forced response.

### Initial Conditions

Initial conditions

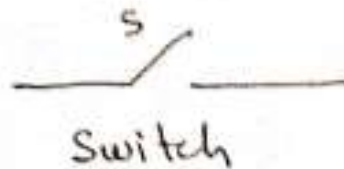

- (i) At  $t=0$ , switches are operative make
- (ii) At  $t=0^-$ , it is the time just before closing the switch i.e. switch is about to close.
- (iii) At  $t=0^+$ , it is the time just after ~~it~~ immediately closing the switch


### III. TRANSIENTS

### Initial Conditions

(1) Resistor (R) :

→ The property of resistor is to oppose the flow of current.

Case (1) : At  $t = 0^-$  :

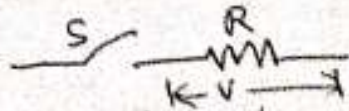


when switch is opens, the current doesn't flow.

Hence,  $I = 0$

Case (2) : At  $t = 0^+$  [Transient State]

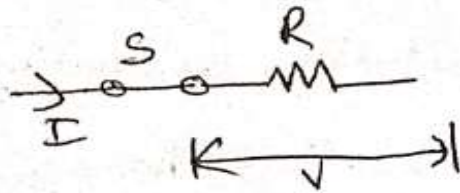$t = 0^+$  means, the time just immediately after closing switch.



Hence


$$V = IR$$

$$I = \frac{V}{R}$$


### III. TRANSIENTS
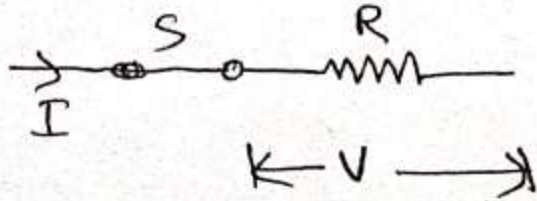
### Initial Conditions

Case (3) : At  $t = \infty$  [steady state]



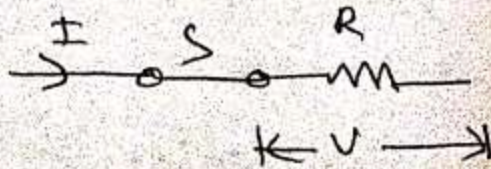$t = \infty$  means, the current flows continuously to resistor  
Then at infinity time



$$V = IR$$


$$I = \frac{V}{R}$$

### III. TRANSIENTS

### Initial Conditions


(2) Inductor (L)

→ Property of inductor is it opposes the sudden change in current

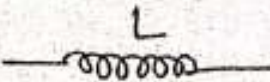Symbol 

Case (1): At  $t=0^-$

At  $t=0^-$  means switch is open

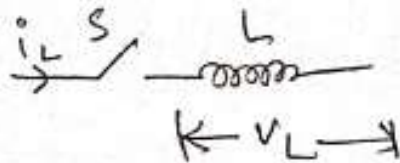

under this conditions,  $i_L = 0$


Hence  $\boxed{t=0^-, i_L=0}$

### III. TRANSIENTS
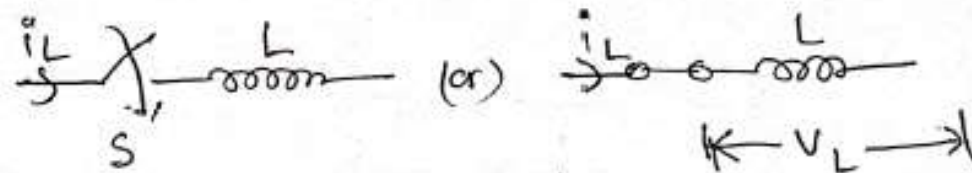
### Initial Conditions

Case (2): At  $t=0^+$  [Transient state]


- At  $t=0^+$  means it is the time just immediately after closing the switch.



- But due to inductor property, it doesn't allow sudden change in current.

Hence  $t=0^+, i_L=0$ ,  $V_L = \text{Full voltage}$

- Hence Inductor acts as open circuit

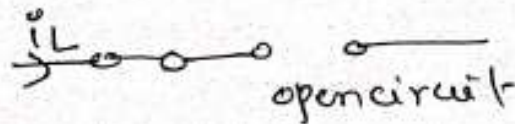


### III. TRANSIENTS
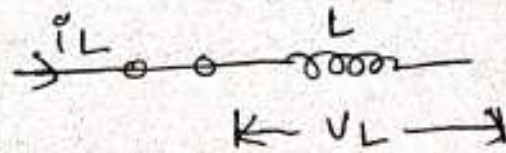
### Initial Conditions

Case (3): At  $t = \alpha$  (Steady state)


- when current flows continuously, then full current flows in the inductor.



$$\text{At } t = \alpha, \quad i_L = i_{\text{Full current}}$$

$$V_L = 0$$

→ Hence, Inductor acts as short circuit

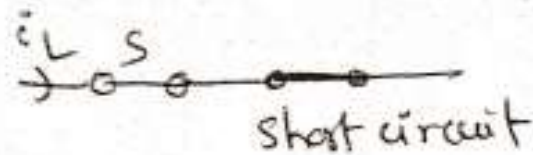

### III. TRANSIENTS


### Initial Conditions

(3) capacitor (C)

The property of capacitor is it doesn't allow sudden change in voltage.

case (1): At  $t = 0^-$

when switch is open

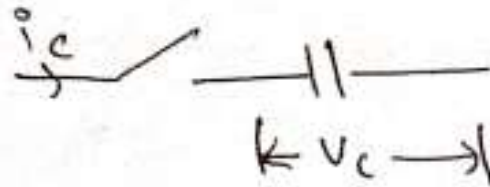

Hence,


$$t = 0^-, V_c = 0$$

### III. TRANSIENTS
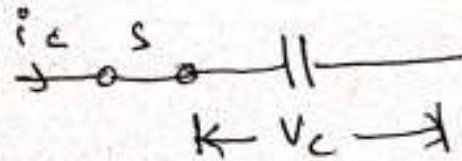
### Initial Conditions

case(2): At  $t=0^+$  [Transient state]


→  $t=0^+$ , means after immediately closing switch



→ But due to property of capacitor,

$$\boxed{\text{At } t=0^+, V_c=0}$$

→ Hence, it acts as short circuit

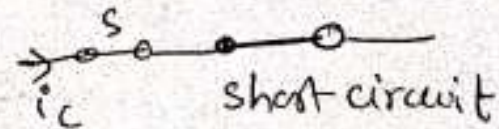


### III. TRANSIENTS
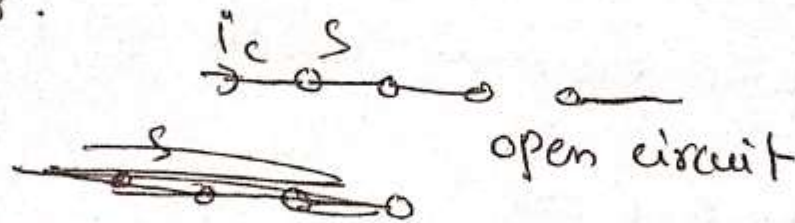
### Initial Conditions

Case(3): At  $t = \infty$  (steady state)

→ under this conditions, Full voltage appears across the capacitor.












→ At  $t = \infty$ ,  $v_c = V_{\text{full voltage}}$   $\therefore i_c = 0$

→ Hence capacitor acts as open circuit.

# III. TRANSIENTS

# Initial Conditions

## Summary

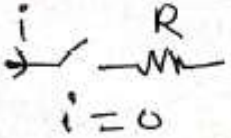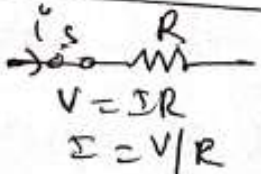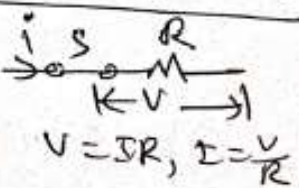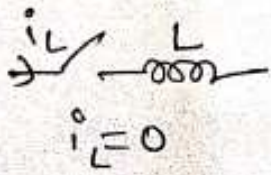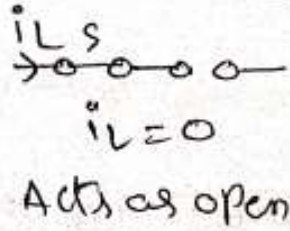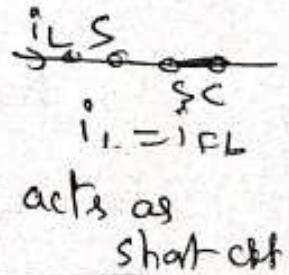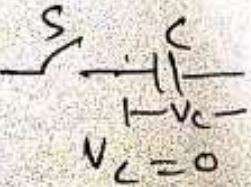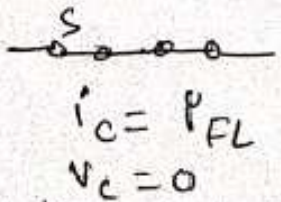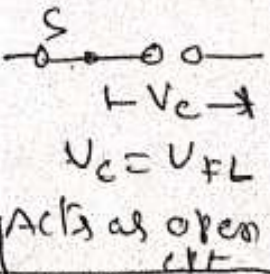Parameter	At $t=0^-$	At $t=0^+$ (Transient state)	At $t=\infty$ (Steady state)
Resistor (R)	 <p><math>i = 0</math></p>	 <p><math>V = IR</math> <math>I = V/R</math></p>	 <p><math>V = IR, I = \frac{V}{R}</math></p>
Inductor (L)	 <p><math>i_L = 0</math></p>	 <p><math>i_L = 0</math> Acts as open circuit</p>	 <p><math>i_L = I FL</math> acts as short circuit</p>
Capacitor (C)	 <p><math>V_C = 0</math></p>	 <p><math>V_C = 0</math> Acts as short circuit</p>	 <p><math>V_C = V FL</math> Acts as open circuit</p>


# III. TRANSIENTS

# Differential Equations

## First order differential equations

Generally KVL is applied to circuit containing R-L, R-C and R-L-C elements which gives differential equations

For eg: Take R-L ckt

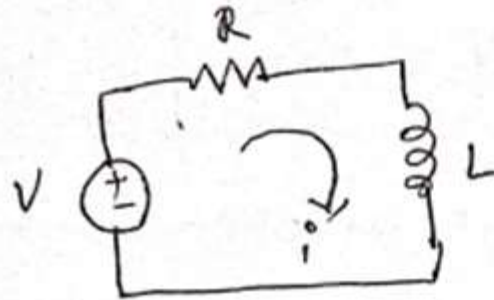

KVL is applied to the ckt

$$V = IR + L \frac{di}{dt}$$

$$\therefore \frac{di}{dt} + \frac{R}{L}i = \frac{V}{L} \quad \text{--- (1)}$$

eq (1) is first order differential equation.

The solution of the differential equation is obtained by two ways.

- ① Differential equations (D.E) method
- ② Laplace transform method

#### ① D.E method

In this method, the differential equations are of two types

- ① Non-homogeneous D.E
- ② Homogeneous D.E

### III. TRANSIENTS

### Differential Equations

1) Non-homogeneous DE method

In this method, the General equation is

$$\frac{di}{dt} + P I = Q \quad (2)$$

The solution is

From the example

$$P = \frac{R}{L}, \quad Q = \frac{V}{L}$$

$i(t) = \text{complementary function} + \text{Particular Integral}$

= Transient response + Steady state

= Natural response + Steady state

$$= i_{CF} + i_{PI}$$

$$= i_t + i_{ss}$$

$$= K e^{-Pt} + e^{-Pt} \int Q \cdot e^{Pt} dt$$

$$= K e^{-Pt} + e^{-Pt} \cdot Q \cdot \frac{e^{Pt}}{P}$$

$$i(t) = K e^{-Pt} + \frac{Q}{P} \quad \text{Amps}$$

2) Homogeneous DE method

The General equation is

$$\frac{di}{dt} + p i = 0 \quad (3)$$

The solution is

$$\begin{aligned} i(t) &= i_t + i_{ss} \\ &= K e^{-pt} + e^{-pt} \int Q \cdot e^{pt} dt \\ &= K e^{-pt} + 0 \end{aligned}$$


$$\boxed{i(t) = K e^{-pt}} \quad \text{Amps}$$

# III. TRANSIENTS
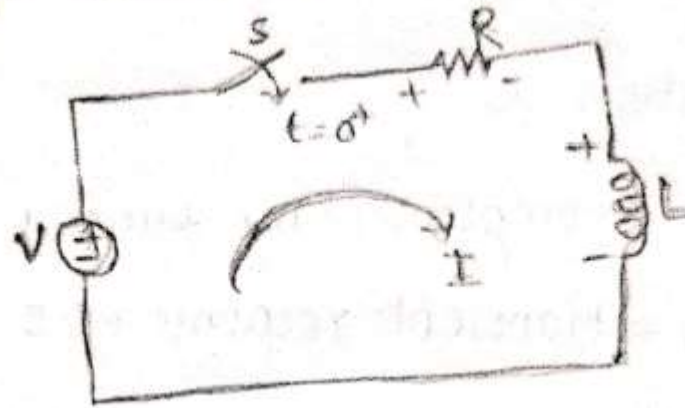
## R-L Circuit

\* Transient Analysis of Series R-L circuit:

Series R-L circuit is excited by DC input which is connected through switch as shown in the figure.



Initial Conditions:

$$t = 0, I = 0 \longrightarrow (1)$$

Now, apply KVL for the closed circuit

$$-V + IR + L \frac{di}{dt} = 0$$

$$V - IR - L \frac{di}{dt} = 0$$

$$V = IR + L \frac{di}{dt}$$

### III. TRANSIENTS

### R-L Circuit

divide both sides with 'L'

$$\frac{di}{dt} + \frac{R}{L}i = \frac{V}{L} \longrightarrow (2)$$

It is a non-homogeneous equation

$$\frac{di}{dt} + Pi = Q, \text{ where } P = \frac{R}{L}, Q = \frac{V}{L}$$

The solution for eqn (2) is

$$i(t) = Ke^{-Pt} + \frac{Q}{P}$$

$$i(t) = Ke^{-\frac{R}{L}t} + \frac{V}{R} \longrightarrow (3)$$

Subst. eqn (1) in eqn (3)

$$0 = Ke^0 + \frac{V}{R}$$

$$\boxed{K = -\frac{V}{R}} \longrightarrow (4)$$

### III. TRANSIENTS

### R-L Circuit

Subst. eqn (4) in eqn (3)

$$i(t) = -\frac{V}{R} e^{-\frac{R}{L}t} + \frac{V}{R}$$

$$\boxed{i(t) = \frac{V}{R} (1 - e^{-\frac{R}{L}t})} \longrightarrow (5)$$

In case of series R-L circuit, the time constant

$$\tau = \frac{L}{R}$$

subst.  $\tau$  in eqn (5)

$$i(t) = \frac{V}{R} (1 - e^{-\frac{t}{\tau}}) \longrightarrow (6)$$

### III. TRANSIENTS

### R-L Circuit

Now,  $t = \tau$ , then

$$i(t) = \frac{V}{R} (1 - e^{-1})$$

$$i(t) = \frac{V}{R} (1 - 0.367)$$

$$i(t) = 0.633 \frac{V}{R}$$

$$\text{at } t = 2\tau, i(t) = \frac{V}{R} (1 - e^{-2}) = 0.865 \frac{V}{R}$$

$$t = 3\tau, i(t) = \frac{V}{R} (1 - e^{-3}) = 0.951 \frac{V}{R}$$


$$t = 4\tau, i(t) = \frac{V}{R} (1 - e^{-4}) = 0.98 \frac{V}{R}$$

$$t = 5\tau, i(t) = \frac{V}{R} (1 - e^{-5}) = 0.99 \frac{V}{R}$$

# III. TRANSIENTS

## R-L Circuit

Now, the graph b/w  $i(t)$  vs  $t$

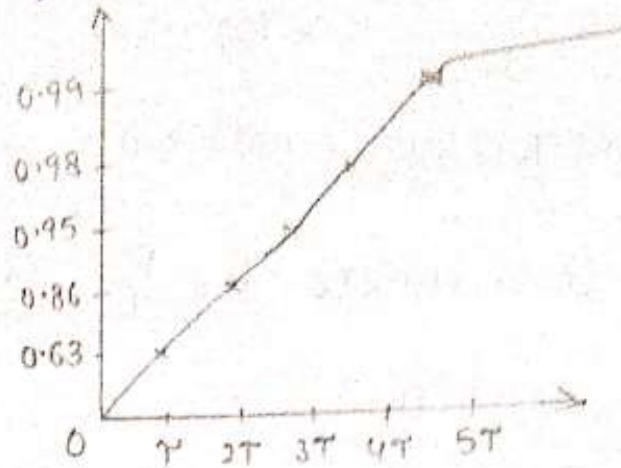

Voltage across resistor:

$$V_R = iR$$
$$= \frac{V}{R} (1 - e^{-\frac{t}{\tau}}) R$$

$$V_R = V(1 - e^{-\frac{t}{\tau}})$$

Voltage across inductor:

$$V = V_R + V_L$$

$$V_L = V - V_R$$

$$= V - V(1 - e^{-\frac{t}{\tau}})$$

$$V_L = Ve^{-\frac{t}{\tau}}$$

### III. TRANSIENTS

### Problems on R-L Circuit

Q: Find the current in series R-L series circuit having  $R=2\Omega$  and  $L=10H$ , while a DC voltage of 100V is applied. What is the value of current after 5 sec of switch ON.

2d: Given that what is the time taken by the current to reach half of its final value.

$$R=2\Omega$$

$$L=10H$$

$$V=100V$$

$$t=5\text{ sec}$$

$$i(t) = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

$$= \frac{100}{2} (1 - e^{-\frac{2}{10}t})$$

$$= 50 (1 - e^{-\frac{1}{5}t})$$

$$\text{at } t=5, \quad i = 50 (1 - e^{-\frac{5}{5}})$$

$$\boxed{i = 31.606 \text{ A}}$$

### III. TRANSIENTS

### Problems on R-L Circuit

$$(i) \text{ Final value of current } i = \frac{V}{R} = \frac{100}{2} = 50 \text{ amp}$$

$$\text{Half of its final value } i = \frac{50}{2} = 25 \text{ amp}$$

$$i = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

$$25 = 50(1 - e^{-\frac{2}{10}t})$$

$$25 = 50(1 - e^{-\frac{t}{5}})$$

$$25 = 50 - 50e^{-t/5}$$

$$-25 = -50e^{-t/5}$$

$$\frac{1}{2} = e^{-t/5}$$

$$\ln\left(\frac{1}{2}\right) = \ln e^{-t/5}$$

$$= -\frac{t}{5}$$

$$t = -5 \ln\left(\frac{1}{2}\right)$$


$$t = -5 \times (-0.693)$$

$$t = 3.46 \text{ sec}$$

### III. TRANSIENTS


### Problems on R-L Circuit

2. In the figure switch 's' is closed and steady state is reached. At  $t=0$ , the switch 's' is opened, find  $i_L(t)$  for  $t > 0$

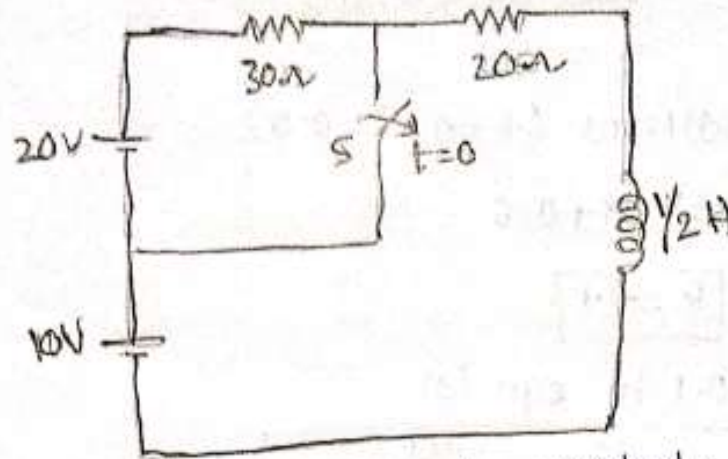


Case 1:

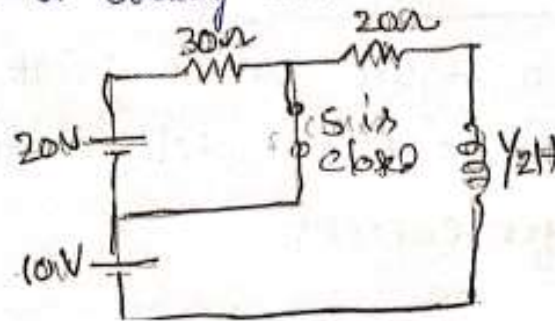Ans: S is closed & steady state is reached:



# III. TRANSIENTS



# Problems on R-L Circuit

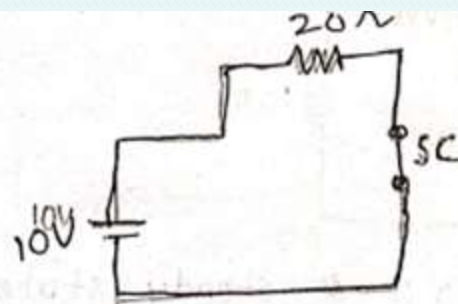

$$i = \frac{V}{R} = \frac{10}{20} = 0.5 \text{ A}$$

Case 2:

At  $t=0$  switch is opened.

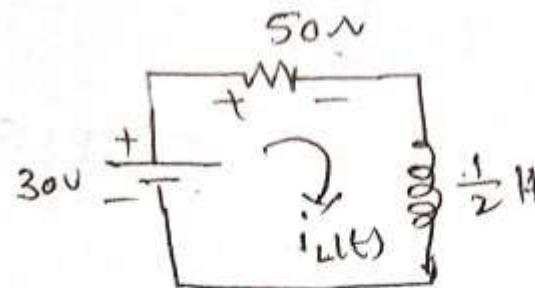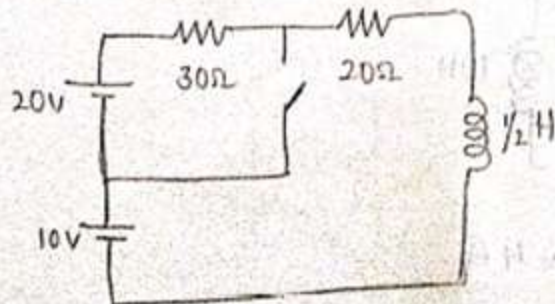

Initial conditions

$$t=0, i = 0.5 \text{ A} \quad (1)$$

Apply KVL to the ckt

$$-30 + 50 i_L(t) + \frac{1}{2} \frac{di_L(t)}{dt} = 0$$

$$50 i_L(t) + \frac{1}{2} \frac{di_L(t)}{dt} = 30$$

$$\frac{di_L(t)}{dt} + 100 i_L(t) = 60 \quad L(2)$$

### III. TRANSIENTS

### Problems on R-L Circuit

It is like a non-homogeneous eqn, the solution is

$$i_L(t) = k e^{-pt} + \frac{Q}{P} \quad [p=100, Q=60]$$
$$= k e^{-100t} + 0.6 \longrightarrow (3)$$

To find  $k$ :

Use initial conditions ( $t=0, i=0.5$ )

$$0.5 = k + 0.6$$

$$k = -0.1$$


Substitute  $k = -0.1$  in eqn (3)

$$i_L(t) = -0.1 e^{-100t} + 0.6$$


### III. TRANSIENTS

### Problems on R-L Circuit

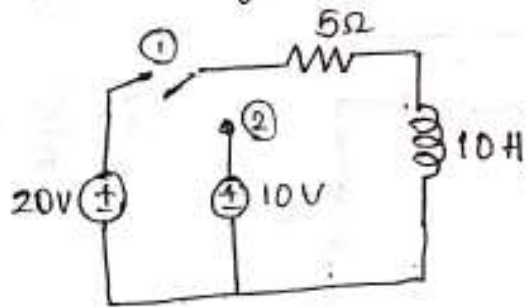3. In the ckt shown in figure switch is at position 1 and steady state is reached. At  $t=0$ , switch is moved to position 2 find the expression for current.



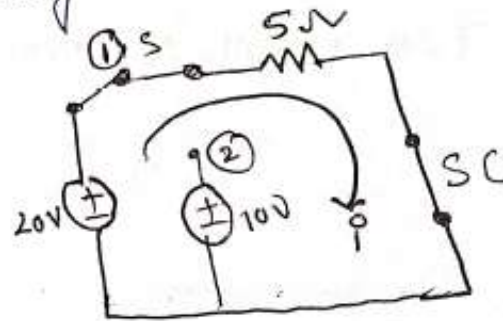Ans: Switch is at position 1 & steady state is reached.




$$i = \frac{V}{R} = \frac{20}{5} = 4 \text{ A}$$

### III. TRANSIENTS
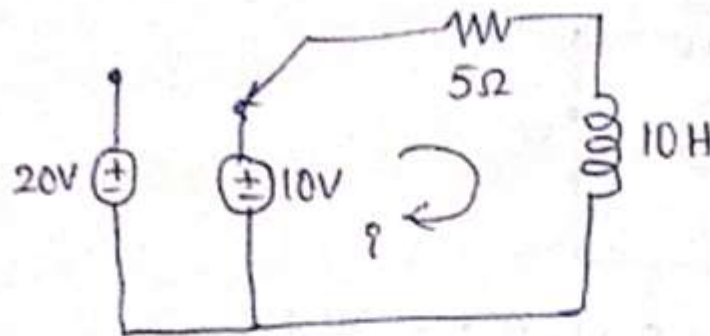
### Problems on R-L Circuit

At  $t=0$ , switch is moved to position 2:



Initial conditions:

$$t=0, i=4A$$

Now, apply KVL to the circuit

$$-10 + 5i + 10 \frac{di}{dt} = 0$$

$$10 \frac{di}{dt} + 5i = 10$$

$$\frac{di}{dt} + \frac{1}{2}i = 1 \longrightarrow (1)$$

### III. TRANSIENTS

### Problems on R-L Circuit

It is like a non-homogeneous eqn, the solution is

$$i(t) = Ke^{-Pt} + \frac{Q}{P} \quad [P = \frac{1}{2}, Q = 1]$$
$$= Ke^{-\frac{t}{2}} + 2 \longrightarrow (2)$$

To find  $K$ :

Use initial conditions,  $(t=0, i=4 \text{ A})$

$$4 = K + 2$$

$$\boxed{K = 2}$$

substitute  $K=2$  in eqn (2)

$$\boxed{i(t) = 2e^{-\frac{t}{2}} + 2.}$$


[III UNIT NT\problem 2 RL.pdf](#)

[III UNIT NT\problem 5 RL.pdf](#)

### III. TRANSIENTS

### Laplace Transform R-L Circuit

Take R-L ckt

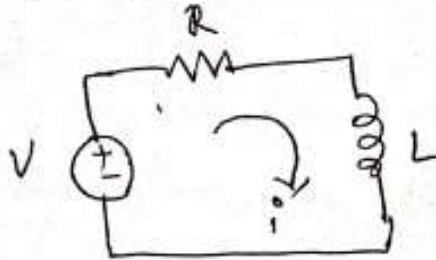

KVL is applied to the ckt

$$V = IR + L \frac{di}{dt}$$

$$\therefore \frac{di}{dt} + \frac{R}{L} i = \frac{V}{L} \quad \text{--- (1)}$$

eq (1) is first order differential equation.

The solution of the differential equation is obtained by two ways.

- ① Differential equations (DE) method
- ② Laplace transform method

### III. TRANSIENTS

### Laplace Transform R-L Circuit

1) Non-homogeneous DE method

In this method, the General equation is

$$\frac{di}{dt} + pI = Q \quad \text{---(2)}$$

The solution is

$$i(t) = Ke^{-pt} + \frac{Q}{p} \quad \text{Amps}$$

2) Homogeneous DE method

The General equation is

$$\frac{di}{dt} + pi = 0 \quad \text{---(3)}$$

The solution is

$$i(t) = Ke^{-pt} \quad \text{Amps}$$

# III. TRANSIENTS

# Laplace Transform R-L Circuit

## Formulas for Laplace Transforms

<u>Formulas</u>		<u>Laplace Transforms</u>		<u>Inverse Laplace Transforms</u>	
<u><math>f(t)</math></u>		<u><math>F(s)</math></u>		<u><math>F(s)</math></u>	<u><math>f(t)</math></u>
1	→	$\frac{1}{s}$		$\frac{1}{s}$	1
v	→	$\frac{v}{s}$		$\frac{v}{s}$	v
t	→	$\frac{1}{s^2}$		$\frac{1}{s^2}$	t
$t^n$	→	$\frac{n!}{s^{n+1}}$		$\frac{n!}{s^{n+1}}$	$t^n$
$e^{-at}$	→	$\frac{1}{s+a}$		$\frac{1}{s+a}$	$e^{-at}$
$e^{at}$	→	$\frac{1}{s-a}$		$\frac{1}{s-a}$	$e^{at}$

### III. TRANSIENTS

### Laplace Transform R-L Circuit

#### Laplace Transforms

$$t \cdot e^{-at} \longrightarrow \frac{1}{(s+a)^2}$$

$$t \cdot e^{at} \longrightarrow \frac{1}{(s-a)^2}$$

$$\sin \omega t \longrightarrow \frac{\omega}{s^2 + \omega^2}$$

$$\cos \omega t \longrightarrow \frac{s}{s^2 + \omega^2}$$

$$\frac{di}{dt} \longrightarrow sI(s) - i(0)$$

$$\int i dt \longrightarrow \frac{I(s)}{s}$$

$$e^{-at} \sin \omega t \longrightarrow \frac{\omega}{(s+a)^2 + \omega^2}$$

$$e^{-at} \cos \omega t \longrightarrow \frac{s}{(s+a)^2 + \omega^2}$$

#### Inverse Laplace Transforms

$$\frac{1}{(s+a)^2} \longrightarrow t \cdot e^{-at}$$

$$\frac{1}{(s-a)^2} \Rightarrow t \cdot e^{at}$$

$$\frac{\omega}{s^2 + \omega^2} \Rightarrow \sin \omega t$$

$$\frac{s}{s^2 + \omega^2} \Rightarrow \cos \omega t$$

$$sI(s) \Rightarrow \frac{di}{dt}$$

$$\frac{I(s)}{s} \Rightarrow \int i dt$$

$$\frac{\omega}{(s+a)^2 + \omega^2} \Rightarrow e^{-at} \sin \omega t$$


# III. TRANSIENTS

## Laplace Transform R-L Circuit

Method 2:

DC transient response analysis of series R-L circuit by

Laplace transform method:

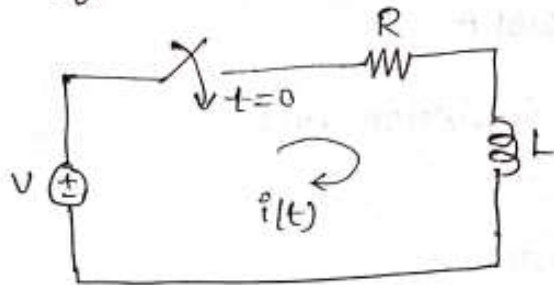

KVL equation,  $-V + IR + L \frac{di}{dt} = 0$

$$V = Ri(t) + L \frac{di(t)}{dt} \rightarrow (1)$$


In Laplace transform

$$L(V) = V/s$$

$$L[i(t)] = I(s)$$

$$L\left[\frac{di(t)}{dt}\right] = sI(s) - i(0) \rightarrow (2)$$

↳ initial condition

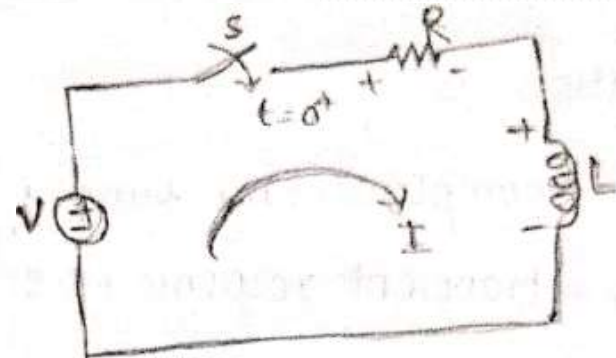

Initial conditions:

$$t=0, i=0$$

### III. TRANSIENTS

### Laplace Transform R-L Circuit

by apply Laplace transform

$$\frac{V}{s} = R I(s) + L [s I(s)]$$

$$I(s) [R + sL] = \frac{V}{s}$$

$$I(s) = \frac{V/s}{R + sL}$$

$$I(s) = \frac{V/s}{L(s + \frac{R}{L})}$$

$$I(s) = \frac{(V/L)}{s(s + \frac{R}{L})} \longrightarrow (3)$$

Using partial fractions,

$$\frac{(V/L)}{s(s + R/L)} = \frac{A}{s} + \frac{B}{s + \frac{R}{L}}$$

$$\frac{A}{s} = \frac{V/L}{s(s + \frac{R}{L})} \Big|_{s=0} = \frac{V/L}{R/L}$$

$$\boxed{A = \frac{V}{R}}$$

### III. TRANSIENTS

### Laplace Transform R-L Circuit

$$\frac{B}{s + R/L} = \frac{V/L}{s(s + R/L)} \Big|_{s = -R/L}$$

$$B = \frac{(V/L)}{-(R/L)}$$

$$B = -\frac{V}{R}$$

from eqn(3)  $I(s) = \frac{V/R}{s} - \frac{V/R}{s + R/L}$

$$= \frac{V}{R} \left[ \frac{1}{s} - \frac{1}{s + R/L} \right] \rightarrow (4)$$


apply inverse Laplace

$$i(t) = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$

### III. TRANSIENTS


### Laplace Transform R-L Circuit

1. In the circuit shown in fig. switch is at position 1 & steady state is reached. At  $t=0$  switch is moved to position 2. Find current through inductor using Laplace transform method.

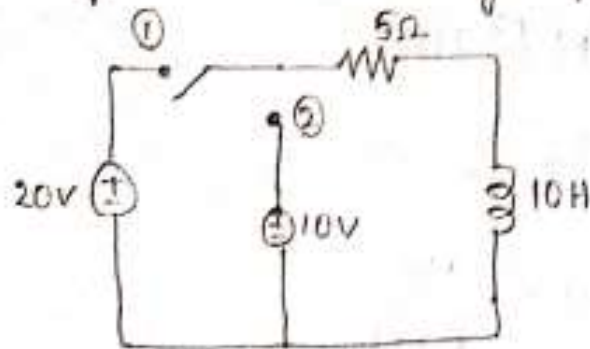

Case 1:

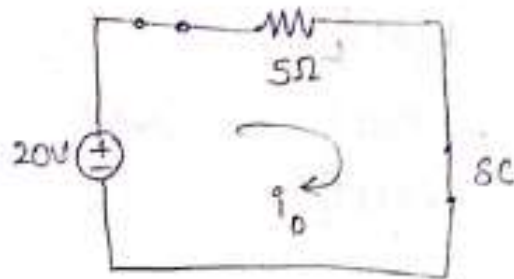Ans: Switch is at position 1 & steady state is reached.




$$i_0 = \frac{20}{5} = 4 \text{ A}$$

### III. TRANSIENTS

### Laplace Transform R-L Circuit

Case 2:

Switch is moved to position 2 at  $t=0$

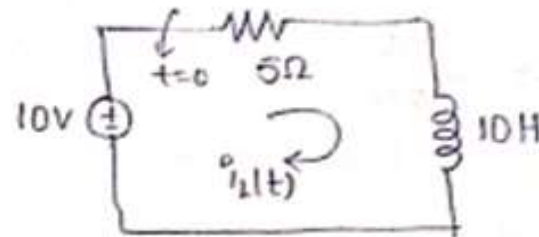

Initial condition,

$$t=0, i_0 = 4A \longrightarrow (1)$$

Apply KVL,

$$-10 + 5i_L(t) + 10 \frac{di_L(t)}{dt} = 0$$

$$10 \frac{di_L(t)}{dt} + 5i_L(t) = 10$$

$$\frac{di_L(t)}{dt} + \frac{1}{2} i_L(t) = 1 \longrightarrow (2)$$

apply Laplace transform,

$$\mathcal{L} \left[ \frac{di_L(t)}{dt} + 0.5 i_L(t) \right] = \mathcal{L} [1]$$

$$[sI(s) - i(0)] + 0.5 I(s) = \frac{1}{s}$$

### III. TRANSIENTS

### Laplace Transform R-L Circuit

$$I(s)(s+0.5) = \frac{1}{s} + 4$$

$$I(s) = \frac{1+4s}{s(s+0.5)} \rightarrow (3)$$

$$\frac{1+4s}{s(s+0.5)} = \frac{A}{s} + \frac{B}{s+0.5}$$

$$\frac{A}{s} = \frac{1+4s}{s(s+0.5)} \Big|_{s=0}$$

$$A = \frac{1+4(0)}{0+0.5}$$

$$\boxed{A = 2}$$

$$\frac{B}{s+0.5} = \frac{1+4s}{s(s+0.5)} \Big|_{s=-0.5}$$

$$B = \frac{1+4(-0.5)}{-0.5}$$

$$= \frac{1-2}{-0.5}$$

$$\boxed{B = 2}$$

$$\therefore I(s) = \frac{2}{s} + \frac{2}{s+0.5}$$

By using inverse Laplace

$$L^{-1} I(s) = L^{-1} \left\{ \frac{2}{s} \right\} + L^{-1} \left\{ \frac{2}{s+0.5} \right\}$$


$$i(t) = 2 + 2e^{-0.5t}$$

$$i(t) = 2(1 + e^{-0.5t})$$

### III. TRANSIENTS

### Laplace Transform R-L Circuit

2 In the following figure, the switch is closed at  $t=0$ , find current through inductor using Laplace transform method.

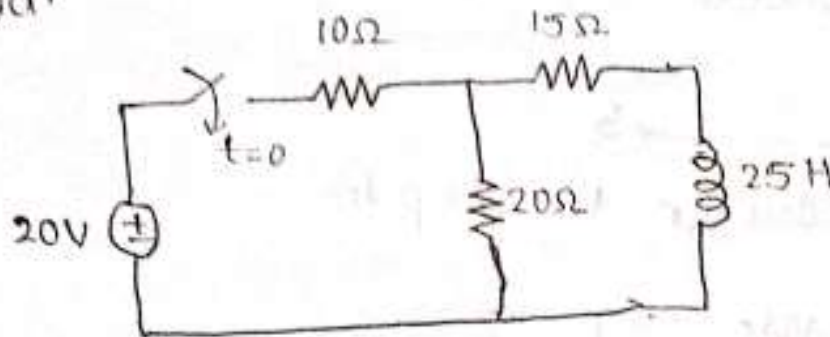


Case 1:

Ans. Initial condition,

at  $t=0, i=0 \rightarrow (1)$

Case 2:

Switch is closed at  $t=0$

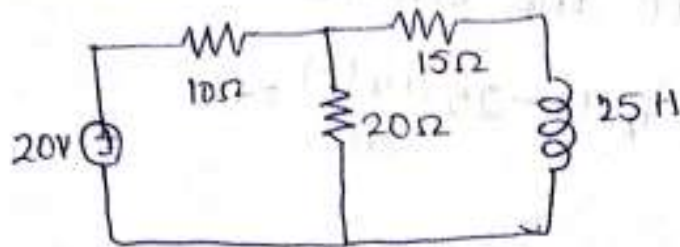


### III. TRANSIENTS
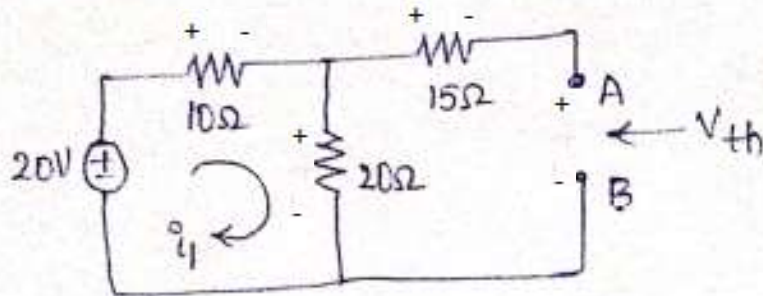
### Laplace Transform R-L Circuit

Apply Thevenin theorem to the above circuit.

Step 1: remove 25 H inductor from the circuit



Step 2: find  $V_{th}$

apply KVL to the closed circuit  $-20 + 10i_1 + 20i_1 = 0$

$$20 - 10i_1 - 20i_1 = 0$$

$$30i_1 = 20$$

$$i_1 = 0.66$$


$$-V_{th} + 20 \times 0.66 = 0$$

$$\boxed{V_{th} = 13.2 \text{ V}}$$

### III. TRANSIENTS
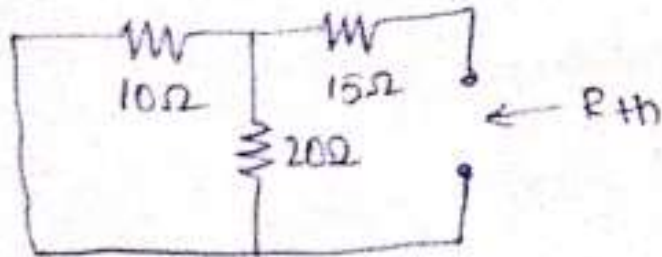
### Laplace Transform R-L Circuit


Step 3: To find  $R_{th}$ , short circuit the voltage source



$$R_{th} = 15 + \frac{10 \times 20}{30}$$

$$R_{th} = 21.66\Omega$$

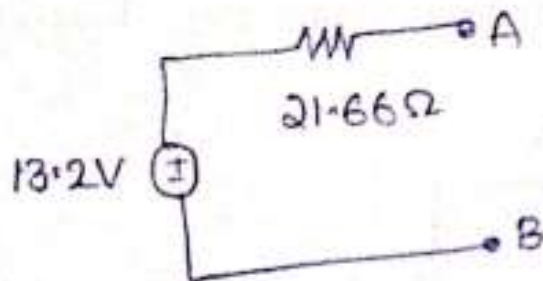
Step 4: Draw thevenin's equivalent circuit



### III. TRANSIENTS

### Laplace Transform R-L Circuit

Step 5: Add 25 H inductor to step 4.

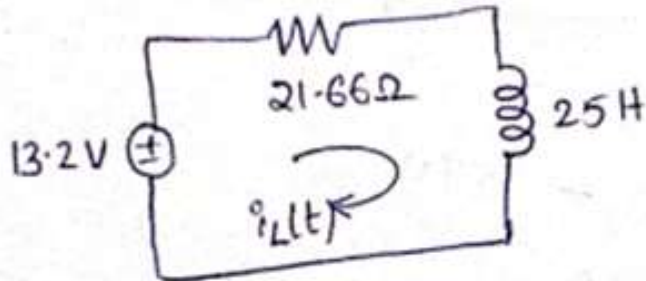

Now apply KVL to the circuit

$$-13.2 + 21.66 i_L(t) + 25 \frac{di_L(t)}{dt} = 0$$

$$13.2 - 21.66 i_L(t) - 25 \frac{di_L(t)}{dt} = 0$$

$$21.66 i_L(t) + 25 \frac{di_L(t)}{dt} = 13.2 \longrightarrow (2)$$

Apply Laplace transform,

$$21.66 i_L(s) + 25 [s i_L(s) - I_L(0)] = \frac{13.2}{s}$$

### III. TRANSIENTS

### Laplace Transform R-L Circuit

$$21.66 i_L(s) + 25 s i_L(s) = \frac{13 \cdot 2}{s}$$

$$i_L(s) [21.66 + 25s] = \frac{13 \cdot 2}{s}$$

$$i_L(s) = \frac{13 \cdot 2}{s(21.66 + 25s)} \quad \text{--- (3)}$$

$$i_L(s) = \frac{\frac{13 \cdot 2}{25}}{s(s + \frac{21.66}{5})}$$

$$i_L(s) = \frac{13 \cdot 2 / 25}{s(s + 0.8664)}$$

$$i_L(s) = \frac{0.528}{s(s + 0.8664)} \quad \text{--- (3)}$$

### III. TRANSIENTS

### Laplace Transform R-L Circuit

$$\text{Let } \frac{0.528}{s(s+0.86)} = \frac{A}{s} + \frac{B}{s+0.86}$$

$$0.528 = A(s+0.86) + Bs$$

$$0.528 = (A+B)s + 0.86A$$

$$A+B=0, \quad A = \frac{0.528}{0.86}$$

$$B = -0.613 \quad A = 0.613$$

$$I_L(s) = \frac{0.613}{s} - \frac{0.613}{s+0.86}$$

apply inverse Laplace transform,

$$i_L(t) = 0.613 [1 - e^{-0.86t}]$$

[III UNIT NT\ADDITIONAL\R-C circuit both methods.pdf](#)

[III UNIT NT\RC Laplace.pdf](#)